


CIRCUIT THEORY

şafak bilici

Power

$$P = V \cdot i$$

$$P = i^2 \cdot R$$

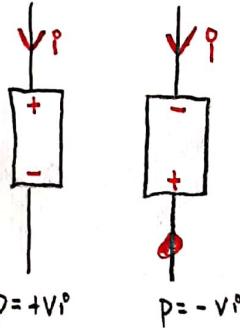

Tellegen's Theorem

$$\sum P = 0$$

$$W = \int_{t_0}^t P dt = \int_{t_0}^t V i dt$$





Kirchhoff's Current Law (KCL)

$$\sum_{n=1}^N i_n = 0$$

Kirchhoff's Voltage Law (KVL)

$$\sum_{n=1}^N V_n = 0$$

Thevenin & Norton

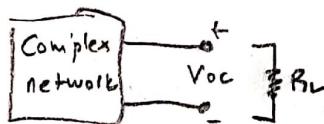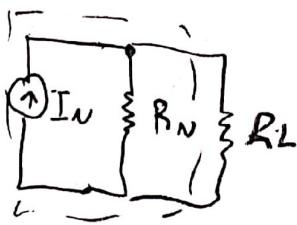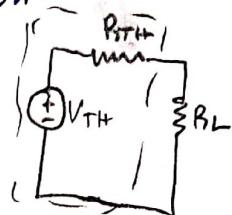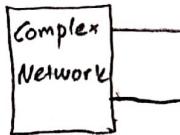

$$V_{oc} = V_{TH} = 8V$$


$$P = V \cdot i = V \cdot \left(\frac{1}{R_L} \cdot \int_{t_0}^{t_1} i_L dt_L + i(t_0) \right)$$

$$L \cdot i_L \cdot \int_{t_0}^{t_1} i_L dt_L$$

$$W = L \cdot \frac{c^2}{2}$$

Circuit Practice

3
 $\frac{12-i}{18-i}$

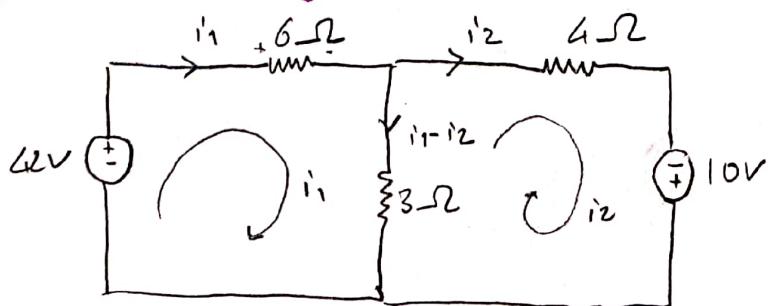


$$6i_1 + 3i_1 - 3i_2 - 4i_2 = 0$$

$$4i_2 - 3i_1 + 3i_2 - 10 = 0$$

$$9i_1 - 3i_2 = 42$$

$$7i_2 - 3i_1 = 10$$

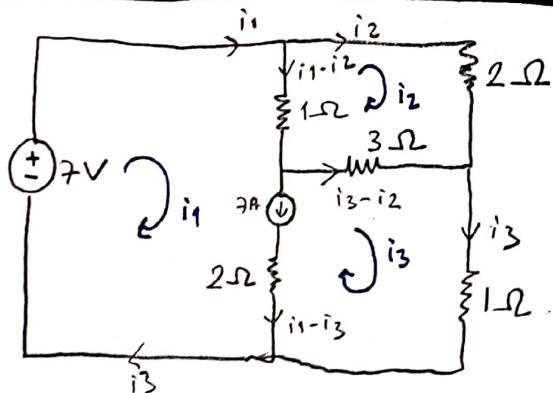


$$2i_2 + 3i_2 - 3i_3 + i_2 - i_1 = 0$$

$$-i_1 + 6i_2 - 3i_3 = 0$$

$$i_1 - i_3 = 7$$

$$i_1 - 4i_2 + i_3 = 7$$

$$i_1 - i_2 + 3i_3 - 3i_2 + i_3$$

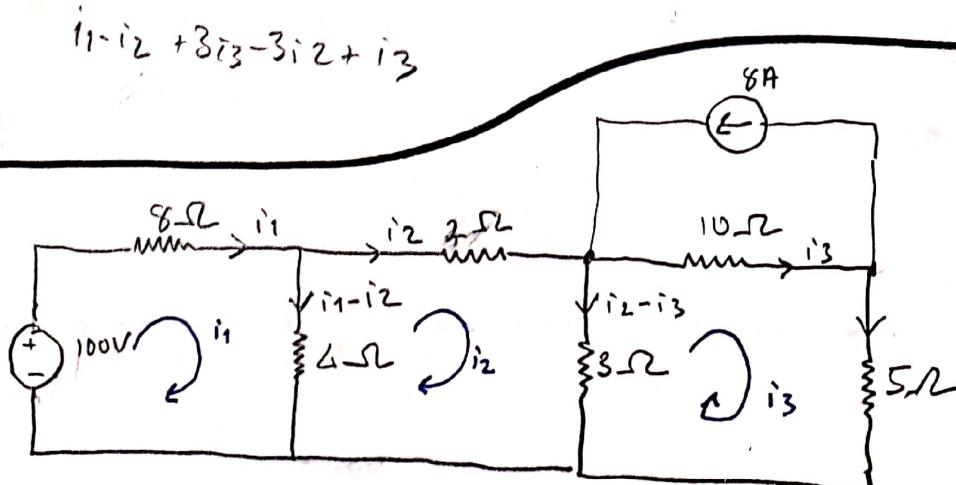

$$8i_1 + 4i_1 - 4i_2 = 100$$

$$2i_2 + 8i_2 - 3i_3 - 4i_1 + 6i_2 = 0$$

$$10i_3 + 5i_3 - 3i_2 + 8i_3 = -100$$

$$12i_1 - 4i_2 = 100$$

$$-4i_1 + 9i_2 - 3i_3 = 0$$

$$-3i_2 + 18i_3 = -100$$


$$|\Delta_i| = 1548$$

$$|\Delta_{i2}| = 4820$$


$$\Delta_i = \begin{bmatrix} 12 & -4 & 0 \\ -4 & 9 & -3 \\ 0 & -3 & 18 \end{bmatrix}$$

$$\Delta_{i2} = \begin{bmatrix} 12 & 100 & 0 \\ -4 & 0 & -3 \\ 0 & -80 & 18 \end{bmatrix}$$

$$\frac{|\Delta_{i2}|}{|\Delta_i|} = \frac{2.79}{1} = i_2$$

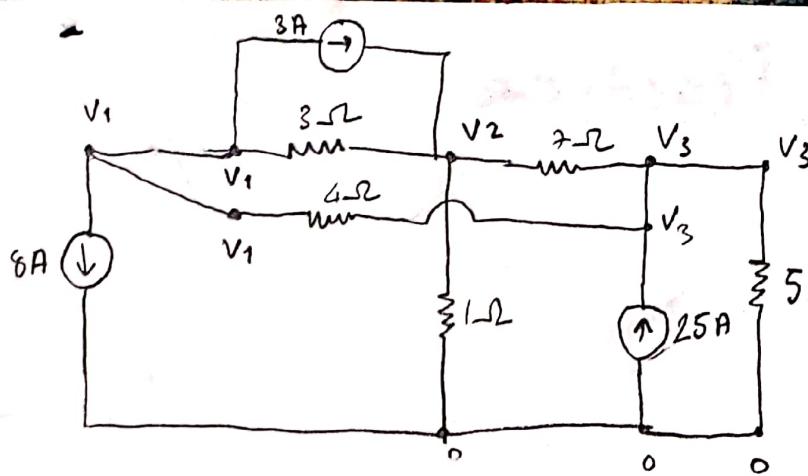

Determine the nodal voltages

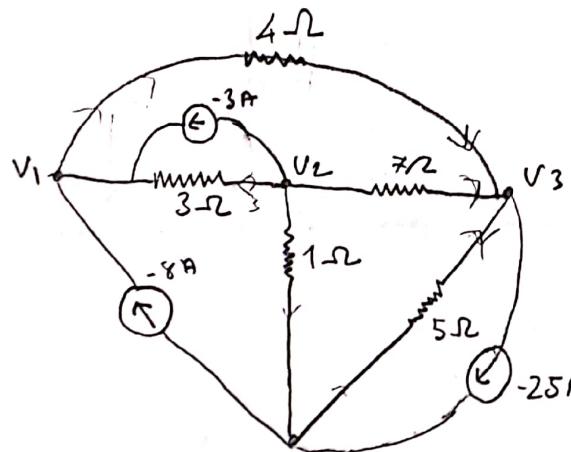


$$-4 = \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{3}$$

$$-3 = \frac{V_1 - V_2}{3} - \frac{V_2}{1} + \frac{V_3 - V_2}{7}$$

$$-25 = -\frac{V_3}{5} + \frac{V_2 - V_3}{7} + \frac{V_1 - V_3}{4}$$

$$3 = \frac{V_2 - V_1}{3} + \frac{V_2}{1} + \frac{V_3 - V_2}{7}$$
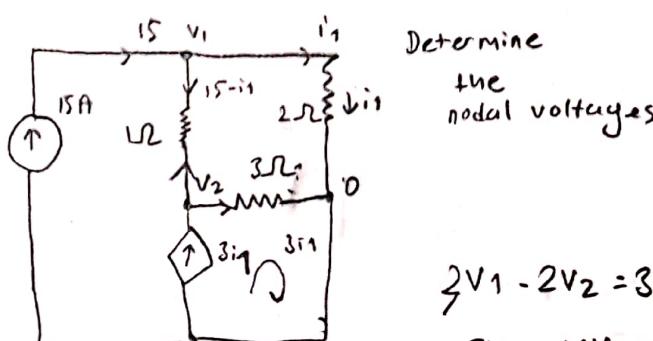
$$25 = \frac{V_3}{5} + \frac{V_3 - V_2}{7} + \frac{V_3 - V_1}{4}$$



Determine
the
nodal voltages

$$i_1 = \frac{V_1}{2}$$

$$2V_1 - 2V_2 = 30$$


$$15V_1 - 8V_2 = 0$$

$$15 = \frac{V_1 - V_2}{1} + \frac{V_1}{2}$$

$$3i_1 = -\frac{V_1 - V_2}{1} + \frac{V_2}{3}$$

$$\frac{3V_1}{2} + \frac{V_1 - V_2}{1} - \frac{V_2}{3} = 0$$

$$9V_1 + 6V_1 - 6V_2 - 2V_2$$

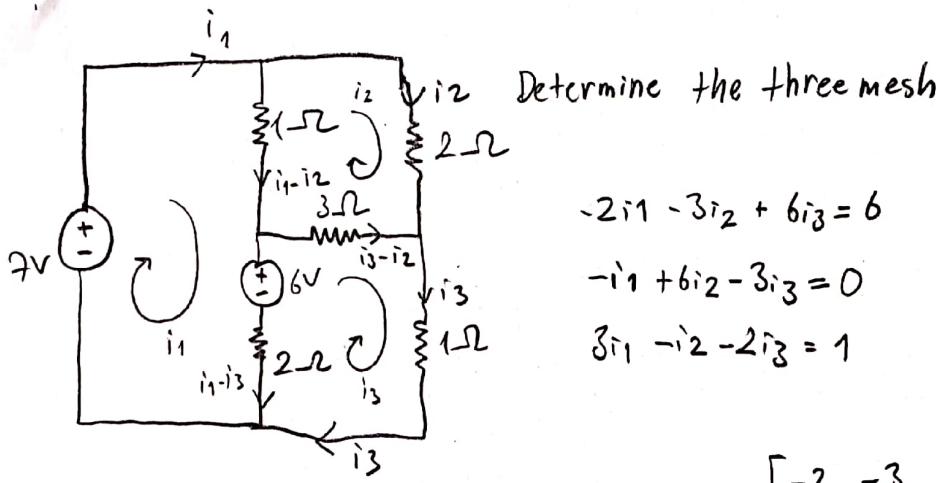

$$3i_3 - 3i_2 + i_3 + 2i_3 - 2i_1 - 6 = 0$$

$$2i_2 + 3i_2 - 3i_3 + i_2 - i_1$$

$$i_1 - i_2 + 6 + 2i_1 - 2i_3 - 7 = 0$$

$$-2i_1 - 3i_2 + 6i_3 = 6$$

$$-i_1 + 6i_2 - 3i_3 = 0$$

$$3i_1 - i_2 - 2i_3 = 1$$


$$\Delta i = \begin{bmatrix} -2 & -3 & 6 \\ -1 & 6 & -3 \\ 3 & -1 & -2 \end{bmatrix}$$

$$\Delta_{i_1} = \begin{bmatrix} 6 & -3 & 6 \\ 0 & 6 & -3 \\ 1 & -1 & -2 \end{bmatrix}$$

$$|\Delta i| = 39$$

$$|\Delta_{i_1}| = -117$$

$$\frac{|\Delta_{i_1}|}{|\Delta i|} = 3$$

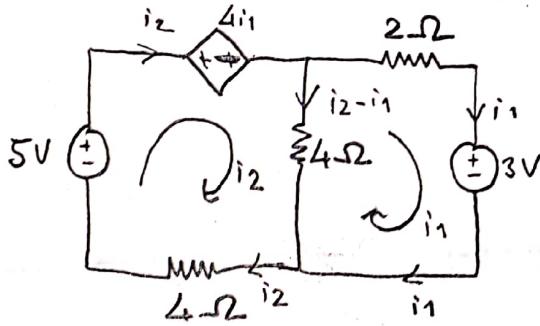

$$4i_1 + 4i_2 - 4i_1 + 4i_2 = 5$$

$$2i_1 + 4i_1 - 4i_2 = -3$$


$$8i_2 = 5$$

$$i_2 = \frac{5}{8} \text{ A}$$

$$6i_1 - 4i_2 = -3$$

$$i_1 = -\frac{1}{12} \text{ A}$$
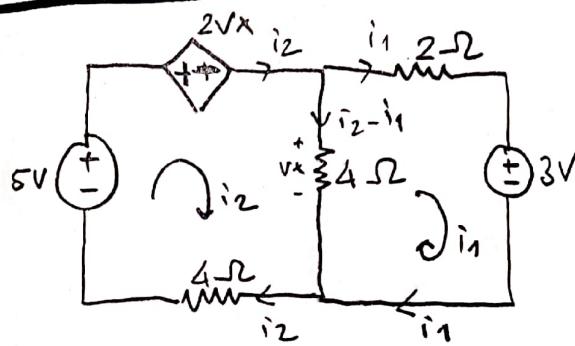
$$\frac{5}{2} - 3 = \frac{-1}{2} = -\frac{1}{12}$$



$$2Vx + 4i_2 - 4i_1 + i_2 = 5$$

$$8i_2 - 8i_1 + i_2 = 5$$

$$2i_1 + 4i_1 - 4i_2 = -3$$

$$Vx = 4 \cdot i_2 - 4i_1$$

$$-8i_1 + 9i_2 = 5$$

$$8i_1 - 4i_2 = -3$$


$$|\Delta i| = -22$$

$$|\Delta_{i_1}| = -47$$

$$i_1 = 1$$

$$\Delta i = \begin{bmatrix} -8 & 9 \\ 8 & -4 \end{bmatrix}$$
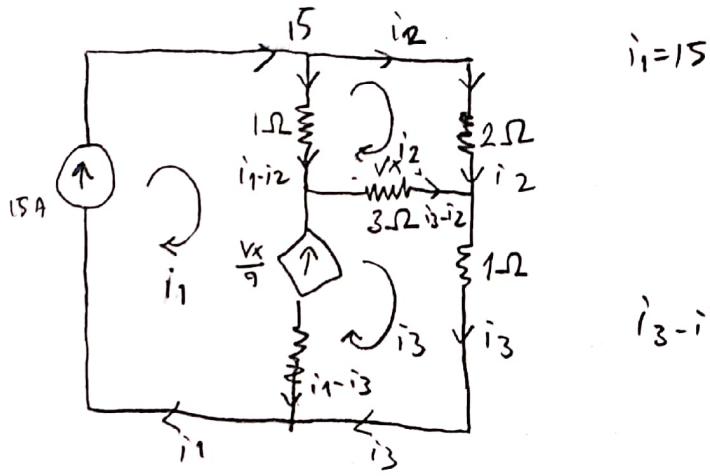
$$\Delta_{i_1} = \begin{bmatrix} 5 & 9 \\ 3 & -4 \end{bmatrix}$$



$$i_1 = 15$$

$$i_3 - i_1 = \frac{V_x}{9} = \frac{3(i_3 - i_2)}{9}$$


$$\frac{1}{3}(i_3 - i_2) = i_3 - i_1$$

$$1 - \frac{1}{3}$$


$$-i_1 + \frac{2i_3}{3} + \frac{1i_2}{8} = 0$$

$$\boxed{\frac{2}{3}i_3 + \frac{1}{8}i_2 = 15}$$

$$2i_2 + 3i_2 - 3i_3 + i_2 - i_1$$

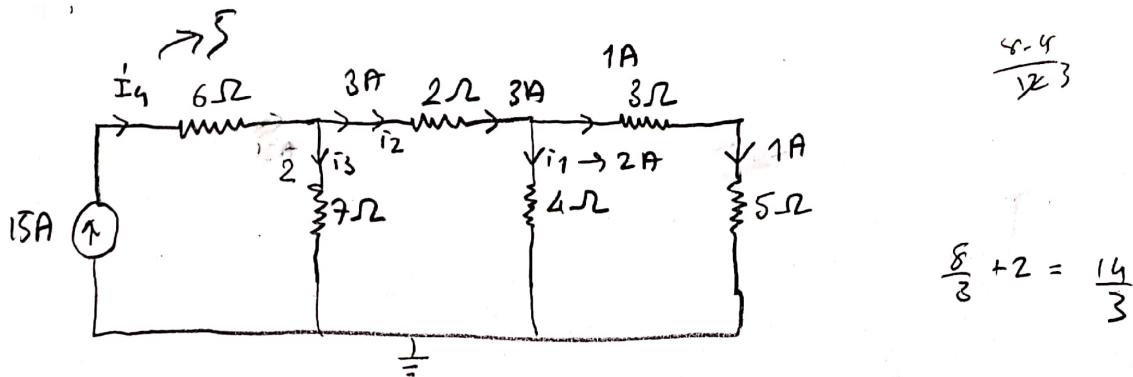

$$\frac{14}{3} \cdot 3$$

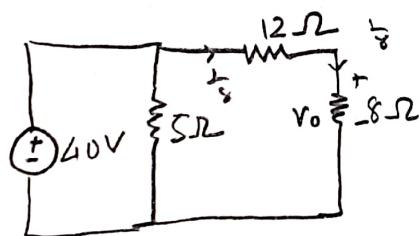


$$V_o = 1 \text{ kabul et}$$

Lineerlik kalkülwak V_o bular.


??

$$\frac{6}{20} \cdot \frac{4}{5} = \frac{24}{100} \cdot \frac{1}{8} = 5 \cdot i \quad i = \frac{3}{25}$$


$$\frac{3}{25} + \frac{1}{8}$$

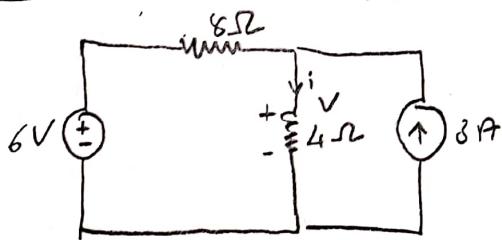

find V with superposition theorem

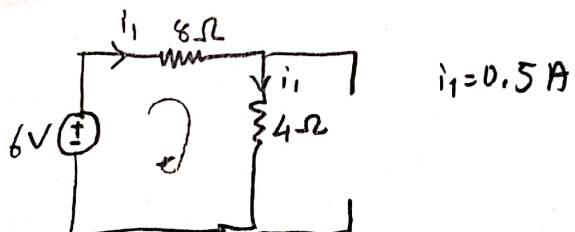


~

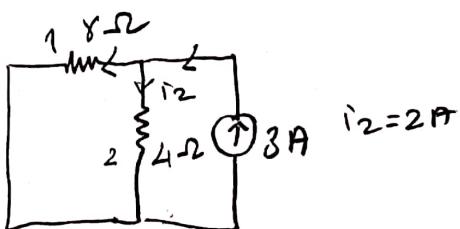


$$i = i_1 + i_2 = 2.5 \text{ A}$$

$$V = 4 \cdot (2.5) = 10 \text{ V}$$

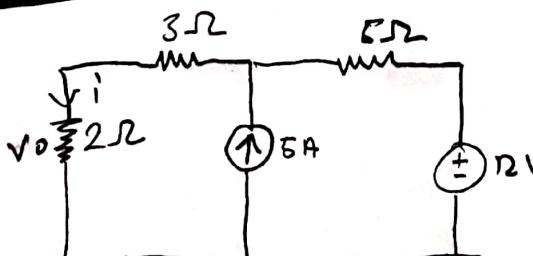




$$V_0 = 2$$

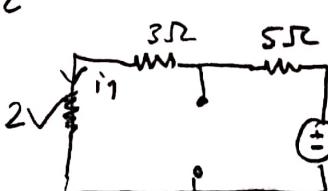

$$i_1 = \frac{1}{2} \cdot 2 = 1 \text{ A}$$

$$3.7 \times 2 = 7.4$$

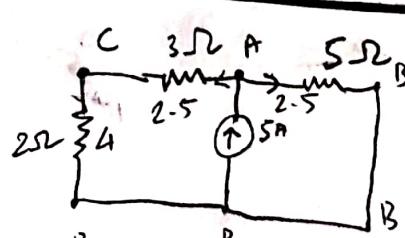

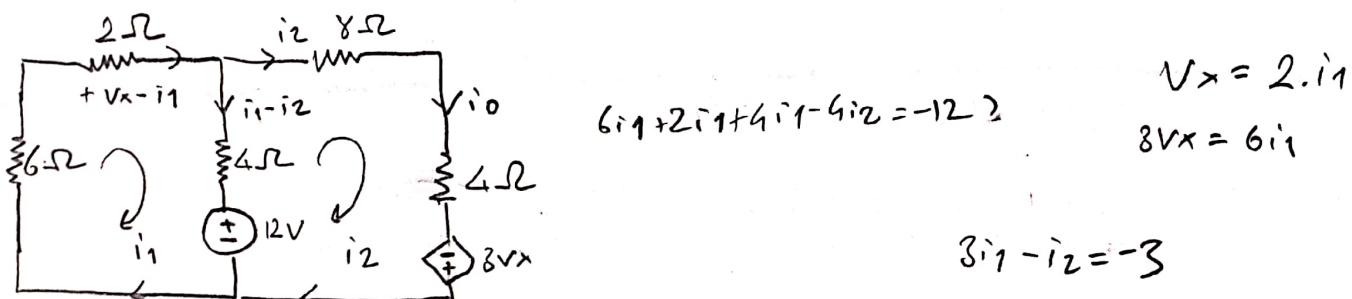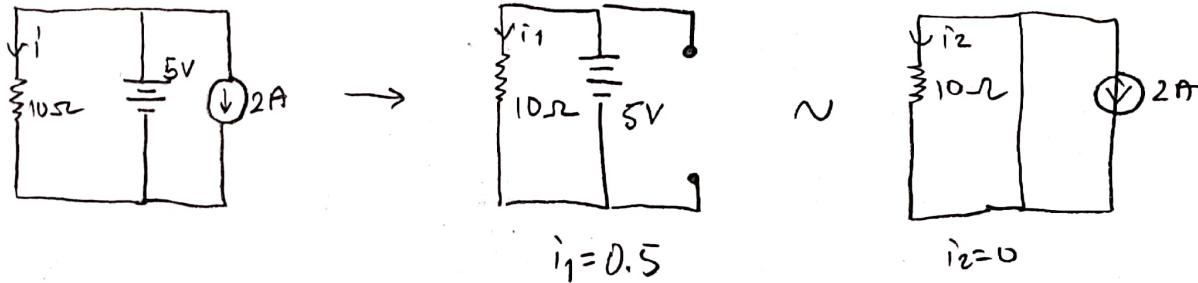


$$8i_2 + 4i_2 - 6i_1 + 4i_2 - 4i_1 = 12$$

$$12i_2 - 10i_1 = 12$$

$$\Delta_i = \begin{bmatrix} 3 & -1 \\ -5 & 8 \end{bmatrix} \Delta_{12} \begin{bmatrix} 3 & -3 \\ -5 & 6 \end{bmatrix}$$


$$\frac{|\Delta_{12}|}{|\Delta_i|} = \frac{3}{19}$$

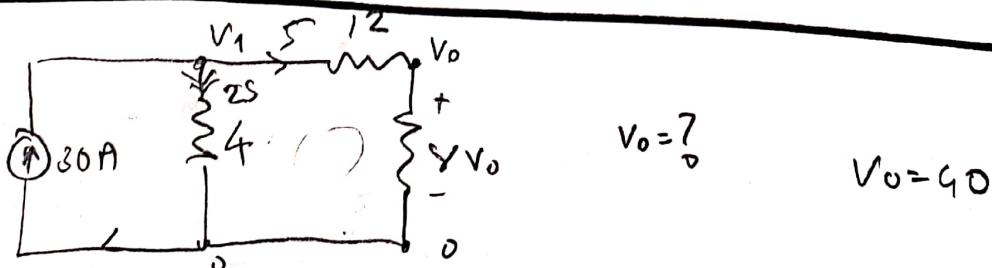


$$20 = \frac{V_1}{4} + \frac{V_1}{20}$$

$$\frac{6V_1}{20} = 20$$

$$V_1 = 100$$

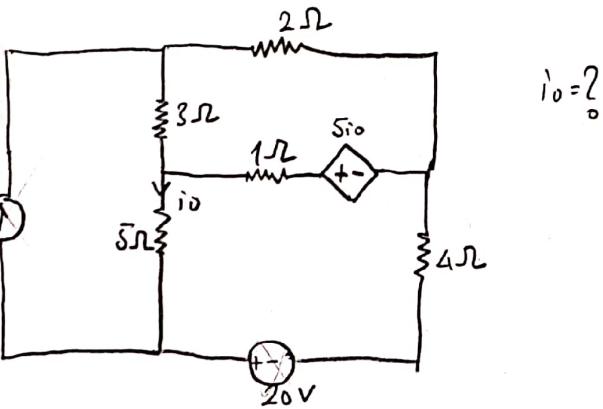

Superposition

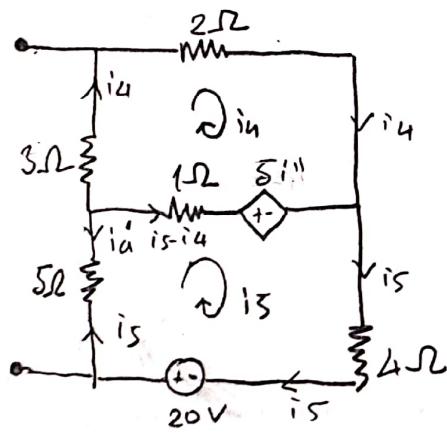

$$-20 + 5i_5 + 5i'' + i_5 - i_4 + 4i_5$$

$$10i_5 - i_4 - 5i'' = 20$$

$$3i_4 + 2i_4 + i_4 + i_5 + 5i'' = 0 \quad i_5 = -i''$$

$$\begin{aligned} 6i_4 - i_5 - 5i'' &= 0 \\ 6i_4 &= 4i'' \end{aligned}$$


$$+ 5i'' - i_4 = 20$$

$$-4i'' + 6i_4 = 0$$

$$\Delta i = \begin{bmatrix} 5 & -1 \\ -4 & 6 \end{bmatrix} \quad \Delta i'' = \begin{bmatrix} 20 & -1 \\ 0 & 6 \end{bmatrix}$$

$$|\Delta i| = -c$$

$$|\Delta i''| = \frac{-60}{17} \text{ A}$$

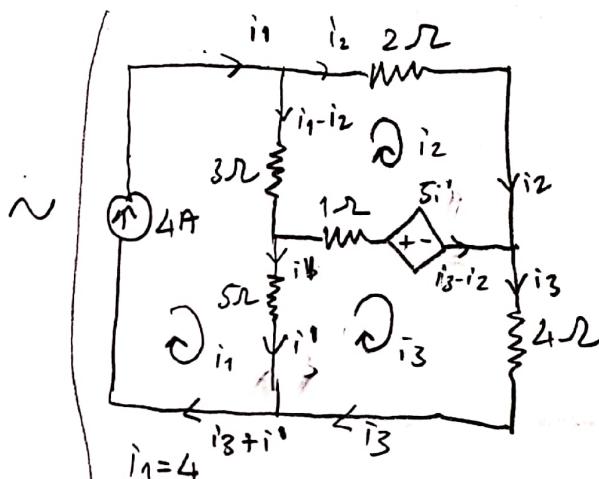

$$i'' = 4 - i_3$$

$$i_3 + i'' = i_1 = 4$$

$$3i_2 - 3i_1 + 2i_2 - 5i'' + i_2 - i_3 = 0$$

$$-8i_1 + 6i_2 - i_3 - 5i'' = 0 \quad 6i_2 - i_3 - 5i'' = 12$$

$$i_3 - i_2 + 4i_3 - 5i'' + 5i'' = 0$$

$$6i_2 - i_3 - 20 + 5i_3 = 12$$

$$5i_3 - i_2 = 0$$

$$6i_2 + 6i_3 = 32$$

$$4i_3 + 6i_2 = 32$$

$$|\Delta x| = 34$$

$$\frac{32}{84} = i_3$$


$$4 - \frac{32}{84}$$

$$\frac{32}{84} = \frac{16}{42} = \frac{8}{21}$$


$$\frac{52}{17}$$

$$\frac{52}{17} - \frac{60}{17} = i'' + i''' = \frac{-8}{17}$$

Thévenin


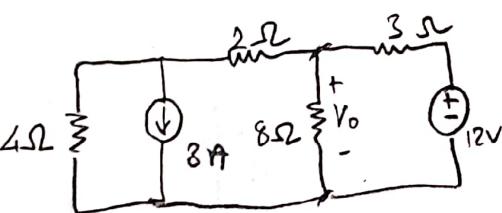


use source transformation to find
V_o

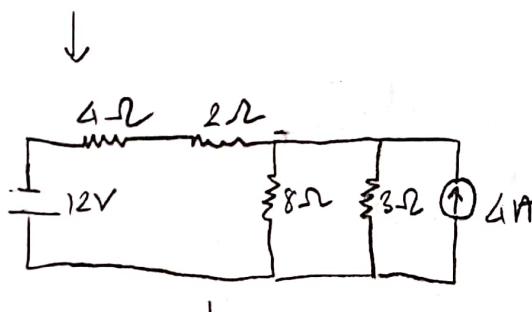


$$5k = 2A$$

$$k = \frac{2}{5} A$$

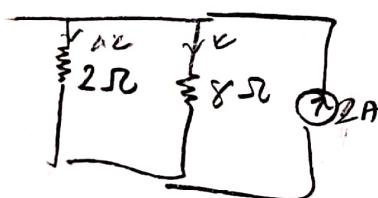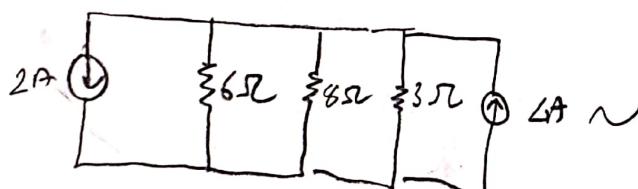

$$\frac{1}{5} \cdot Y = 8.2 V$$

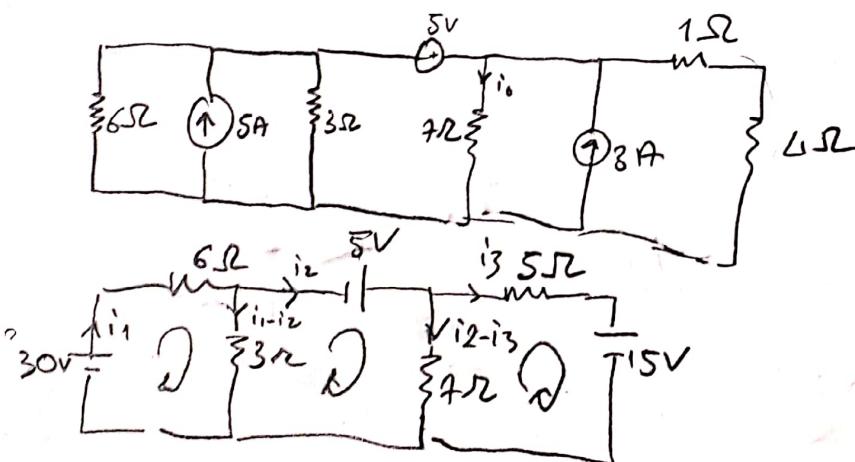

use source transformation
to find i_o

??

??

$$9i_1 - 3i_2 = 80$$

$$-3i_1 + 3i_2 = 5$$

$$-7i_2 + 12i_3 = -15$$

$$\Delta_{i_1} = \begin{bmatrix} 9 & -3 & 0 \\ -3 & 3 & 0 \\ 0 & -7 & 12 \end{bmatrix}$$

$$\Delta_{i_3} = \begin{bmatrix} 9 & -3 & 80 \\ -3 & 3 & 5 \\ 0 & -7 & -15 \end{bmatrix}$$

$$\Delta_{i_2} = \begin{bmatrix} 9 & 80 & 0 \\ -3 & 5 & 0 \\ 0 & -15 & 12 \end{bmatrix}$$

$$|\Delta_{i_1}| = 216$$

$$|\Delta_{i_2}| = 1620$$


$$|\Delta_{i_3}| = 675$$

$$\begin{array}{r} 7.500 \\ -3.125 \\ \hline 4.465 \end{array}$$







$$i_2 = 7.5$$



$$i_3 = 3.125$$

Thevenin & Norton

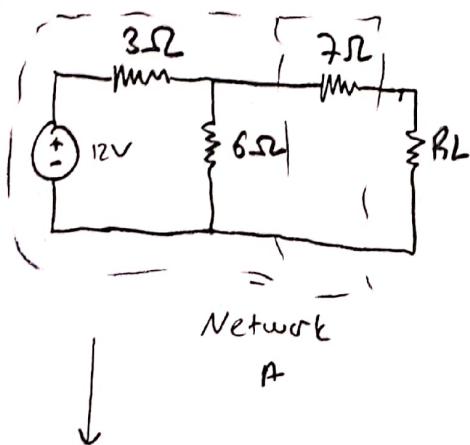

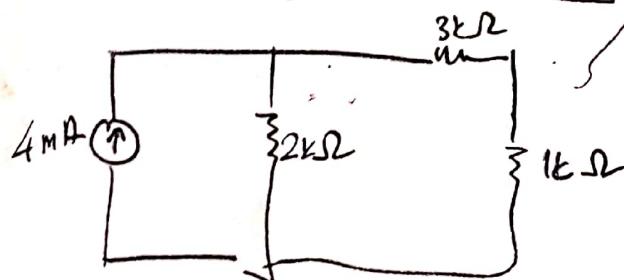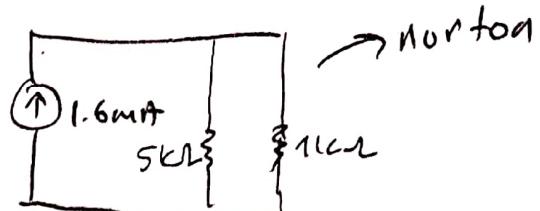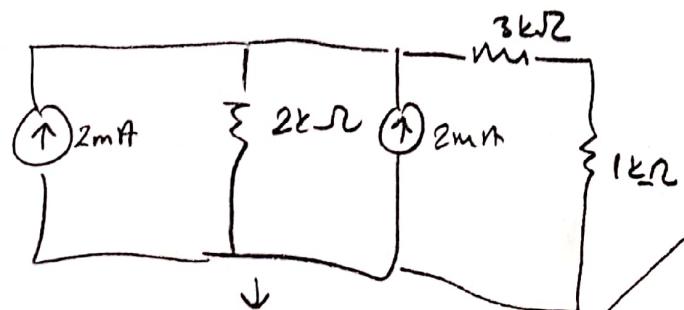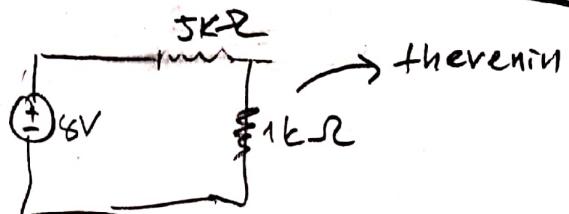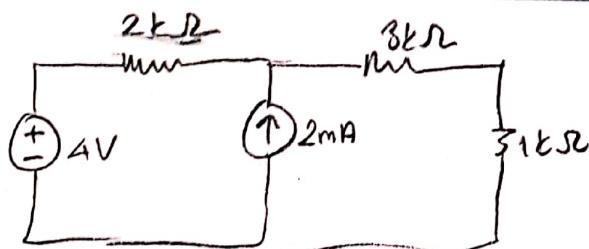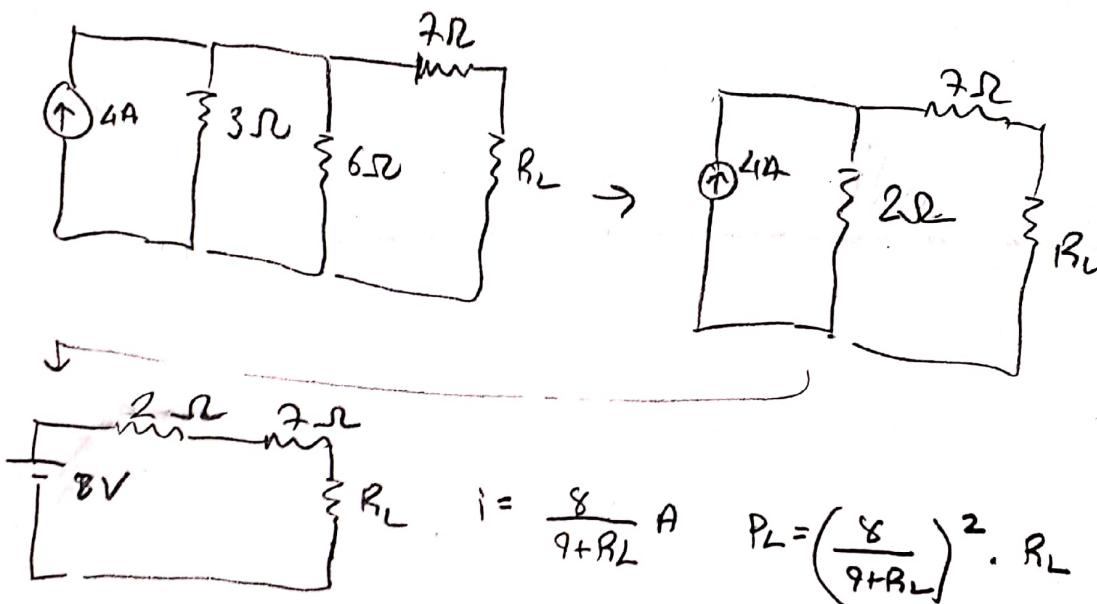Compute the power delivered to the load resistor R_L and determine the Thevenin equivalent of Network A



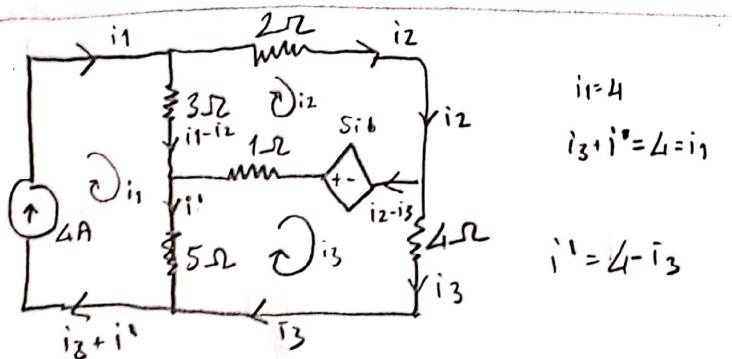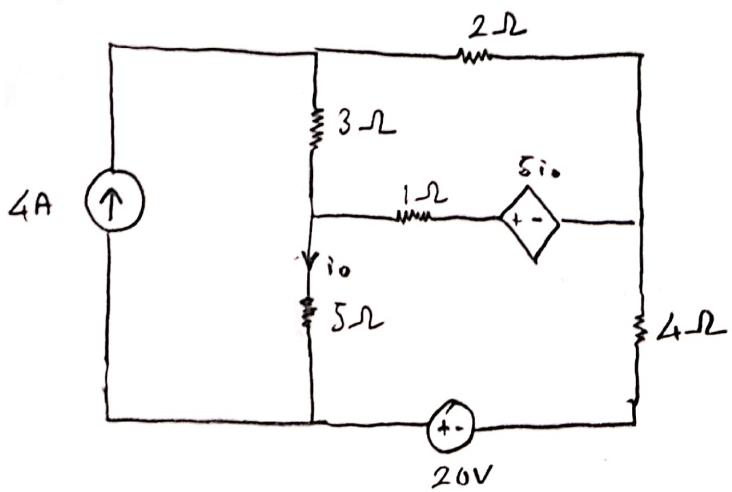


$$2i_2 + i_2 - i_3 + 3i_2 - 3i_1 = 20 - 4i_3$$

$$i_3 - i_2 + 5i^1 + 4i_3 - 5i^1 = 0$$

$$5i_2 + 3i_3 = 20$$

$$-i_2 + 5i_3 = 0$$

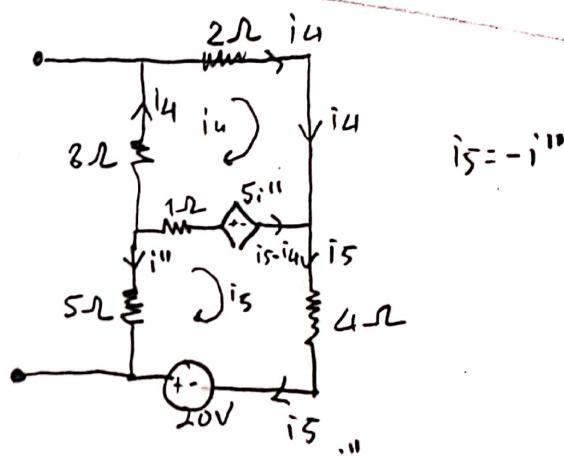

$$2i_4 - 5i^1 + i_4 - i_5 + 3i_4 = 0$$

$$-5i^1 - i^5 + 4i^4 - 4i^5 = 20$$

$$6i_4 - 4i^1 = 0$$


$$6 \times -i_4 - 10i^1 = 20$$

RC and RL

RC circuit

Suppose that there is some charge on a capacitor at time $t=0$ s.

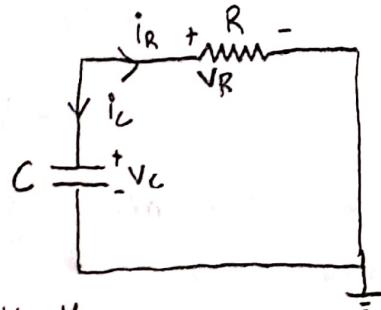This charge could have been stored because a voltage current source had been in the circuit at $t < 0$ s, but was switched off at $t = 0$ s.



$$V_R = V_C$$

$$P_R = -i_C$$

$$i_C = C \cdot \frac{dV_C}{dt}$$

$$i_R = \frac{V_R}{R}$$

$$C \cdot \frac{dV_C}{dt} + \frac{V_R}{R} = 0$$

$$V_R = V_C$$


$$\frac{dV_C}{dt} + \frac{V_C}{RC} = 0$$

$$\frac{dV_C}{dt} \cdot \frac{1}{V_C} + \frac{1}{RC} = 0$$

$$\frac{dV_C}{V_C} = -\frac{dt}{RC} \rightarrow \int \frac{dV_C}{V_C} = \int -\frac{dt}{RC}$$

$$\ln(V_C) = -\frac{t}{RC} + \ln(V_{C0}|_{t=t_0})$$

(1)

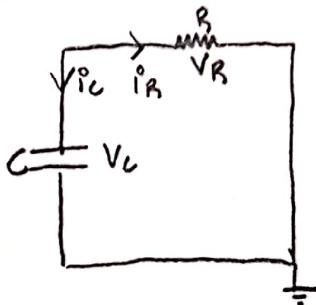

if $V_0 = V_C|_{t=0}$ and $\tau = RC$

$$V_C(t) = V_0 \cdot \exp(-t/\tau) \text{ when } t \geq 0$$

$$I_C = C \cdot \frac{dV_C(t)}{dt}$$

$$I_R(t) = -I_C(t) = \frac{V_0}{R} \cdot \exp(-t/\tau)$$

$$P_R(t) = V_R I_R = \frac{V_0^2}{R} \cdot \exp(-2t/\tau)$$

$$W(t) = \int_0^t P_R(t) dt = \frac{C \cdot V_0^2}{2} \left[1 - \exp(-2t/\tau) \right]$$

$$\begin{aligned} S_n &= 2 \\ n &= 2, 3, 4, \dots \end{aligned}$$

$$\begin{aligned} \frac{1}{60} &= \frac{2}{180} \\ 1 &= \frac{1}{90} \end{aligned}$$

$$\begin{aligned} \frac{1}{50} &= \frac{1}{50} \\ \frac{1}{50} &+ \frac{1}{50} \\ \frac{1}{25} &= \frac{1}{25} \end{aligned}$$


$$\frac{1}{4}$$

(2)


- The initial voltage $V(0) = V_0$ across the capacitor.
 - Can be obtained by inserting DC source to the circuit for a time much longer than τ (at least $t = -5\tau$) and then removing it at $t = 0$.
 - Capacitor
 - open circuit voltage
- The time constant τ .
 - In finding the time constant $\tau = RC$, R is often the Thevenin equivalent resistance at the terminals of the capacitor.
 - That is, we take out the capacitor C and find $R = R_{TH}$ at this terminals

Time Constant

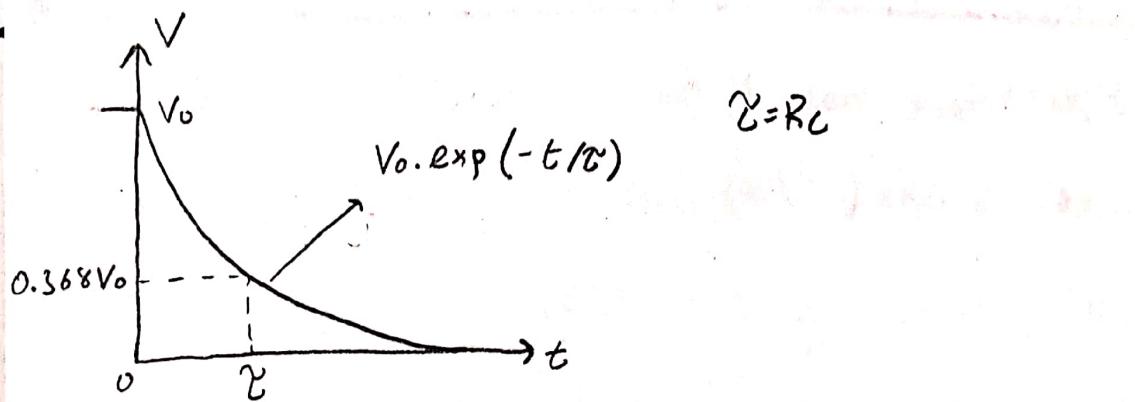The natural response of a capacitive circuit refers to the behavior of the circuit itself, with no external sources of excitation.



RL Circuit

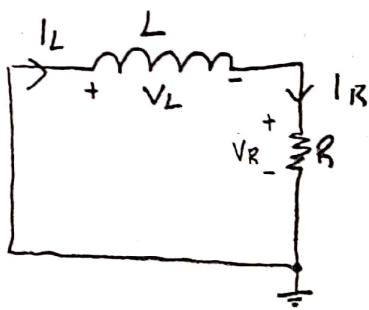

$$I_L = I_R$$

$$V_L + V_R = 0$$

$$V_L = L \cdot \frac{dI_L}{dt}$$

$$I_R = V_R/R$$

$$L \cdot \frac{dI_L}{dt} + R I_R = 0$$


$$\frac{dI_L}{dt} + \frac{R I_L}{L} = 0$$

①

$$\frac{dI_L}{dt} \cdot \frac{1}{I_L} = -\frac{R}{L}$$

$$\frac{dI_L}{I_L} = -\frac{R}{L} dt \rightarrow \int \frac{dI_L}{I_L} = \int -\frac{R}{L} dt$$
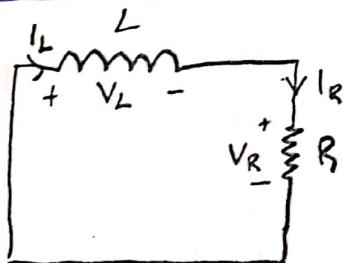
$$\ln(I_L) = -\frac{R}{L} t + \ln(I_{L,t=0})$$



$$\text{if } I_0 = I_L |_{t=0} \text{ and } \gamma = \frac{L}{R}$$






$$I_L(t) = I_0 \cdot \exp(-t/\gamma) \text{ when } t \geq 0$$

$$V_R(t) = -V_L(t) = R \cdot I_0 \cdot \exp(-t/\gamma)$$

$$P_r(t) = V_R I_R = R \cdot I_0^2 \exp(-2t/\gamma)$$

$$W(t) = \int P_r(t) dt = \frac{L I_0^2}{2} \cdot [1 - \exp(-2t/\gamma)]$$

Unit-Step

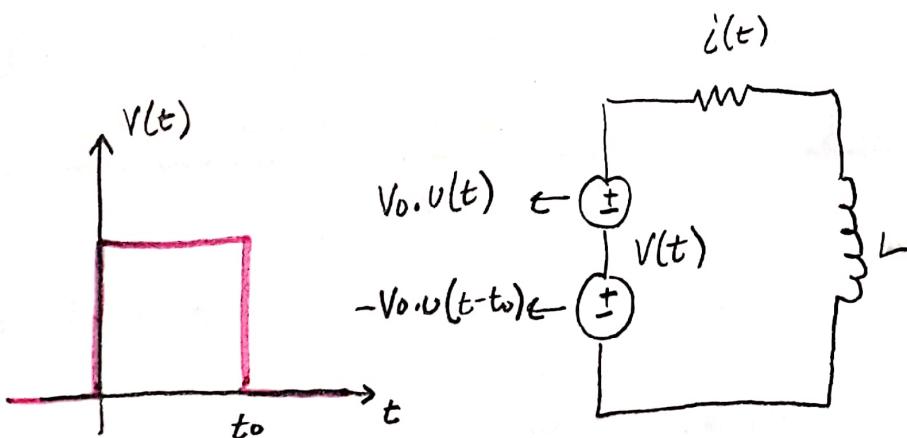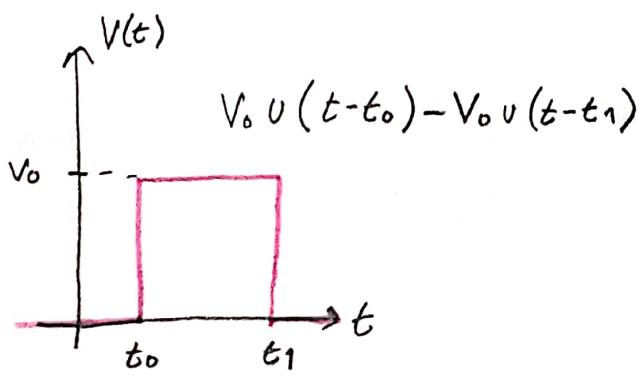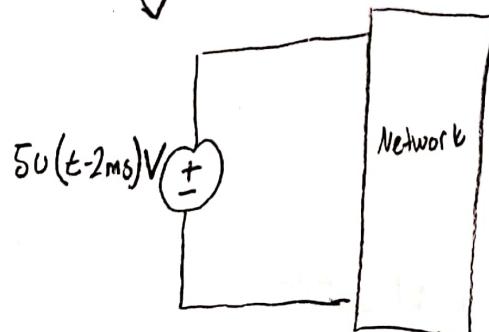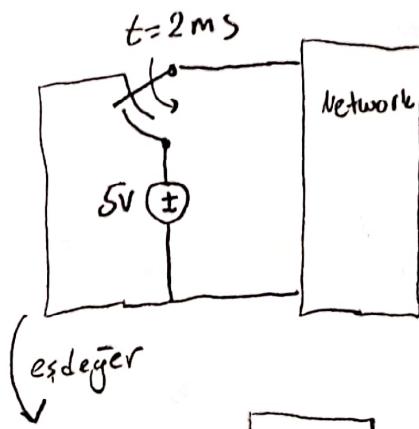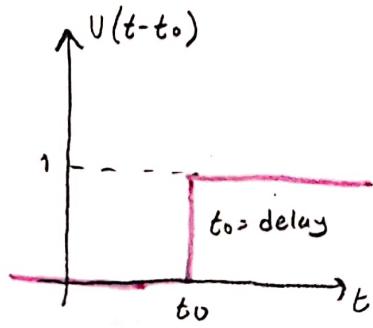

General Equations

RC

$$V_C(t) = V_C(\infty) + [V_C(0) - V_C(\infty)] \cdot e^{-t/\tau}$$

$$I_C(t) = \frac{C}{\tau} [V_C(\infty) - V_C(0)] e^{-t/\tau}$$

$$\tau = RC$$


RL

$$I_L(t) = I_L(\infty) + [I_L(0) - I_L(\infty)] \cdot e^{-t/\tau}$$


$$V_L(t) = \frac{L}{\tau} [I_L(\infty) - I_L(0)] e^{-t/\tau}$$

$$\tau = L/R$$

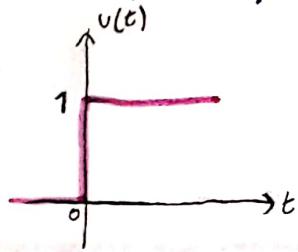
Unit Step Function / Birim Basamak Fonksiyonu



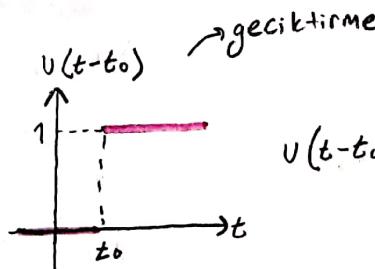
$$u(t) = \begin{cases} 1, & t > 0 \\ \text{nan}, & t=0 \\ 0, & t < 0 \end{cases}$$


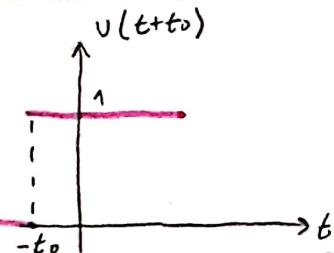
$$u(t-t_0) = \begin{cases} 1, & t > t_0 \\ \text{nan}, & t=t_0 \\ 0, & t < t_0 \end{cases}$$



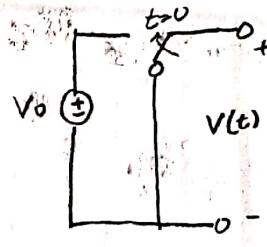
$$u(t+t_0) = \begin{cases} 1, & t > -t_0 \\ \text{nan}, & t=-t_0 \\ 0, & t < -t_0 \end{cases}$$



$$V(t) = \begin{cases} 0V, & t < 0 \\ \text{nan}, & t=0 \\ V_0V, & t > 0 \end{cases}$$

$$V(t) = V_0 \cdot u(t) V$$

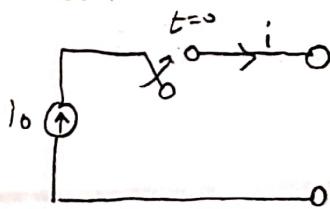


$$i(t) = \begin{cases} 0, & t < 0 \\ \text{nan}, & t=0 \\ i_0, & t > 0 \end{cases}$$

$$i(t) = i_0 \cdot u(t) A$$

Impulse Function / Dörtü Fonksiyonu

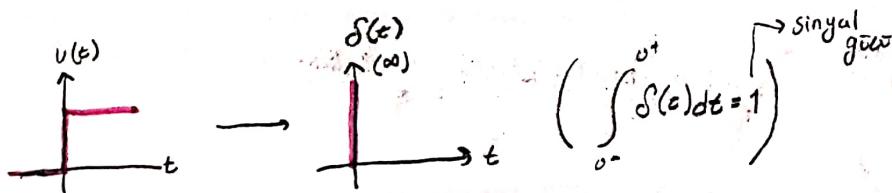
$$\delta(t) = \frac{d}{dt} u(t) = \begin{cases} 0, & t < 0 \\ \text{nan}, & t=0 \\ 0, & t > 0 \end{cases}$$



$$V(t) = V(\infty) + [V(0) - V(\infty)] \cdot \exp(-t/\tau)$$


Genel Formül

Rampa Fonksiyonu

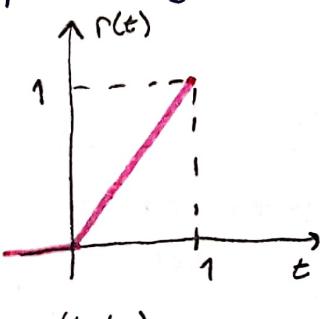



$$r(t) = \int_{-\infty}^t u(\lambda) d\lambda = t \cdot u(t)$$
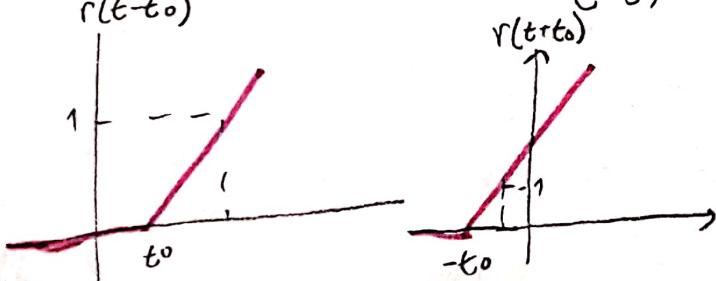
$$r(t) = \begin{cases} 0, & t \leq 0 \\ t, & t \geq 0 \end{cases}$$




$$f = \frac{du(t)}{dt}$$


$$u(t) = \frac{dr(t)}{dt}$$

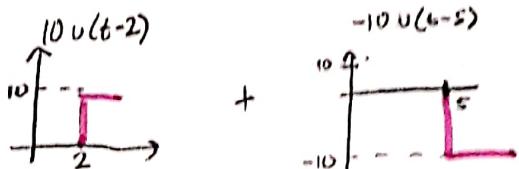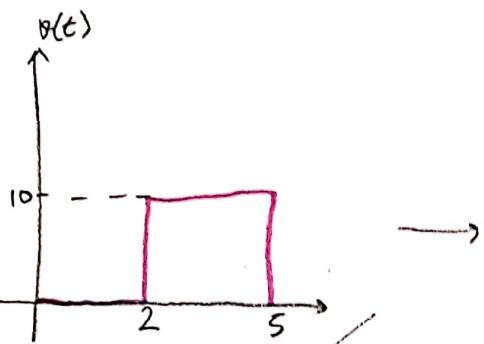


$$v(t) = 10(u(t-2) - u(t-5))$$

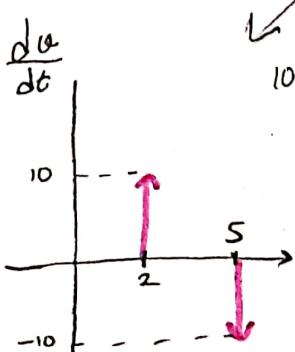


$$10(\delta(t-2) - \delta(t-5))$$

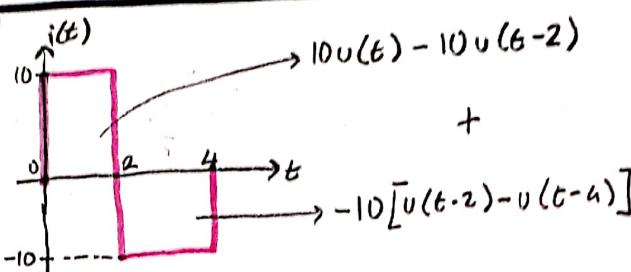

$$i(t) = 10u(t) - 20u(t-2) + 10u(t-4)$$

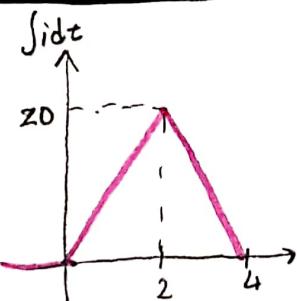

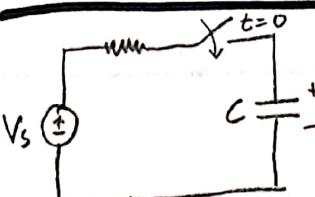
$$r(t) = 10r(t) - 10r(t-2) - 10r(t-4) + 10r(t-6) = 10r(t) - 20r(t-2) + 10r(t-4)$$



$$V_s u(t) = \begin{cases} 0, & t < 0 \\ V_s, & t > 0 \end{cases}$$

$$V(0^-) = V(0^+) = V_0$$

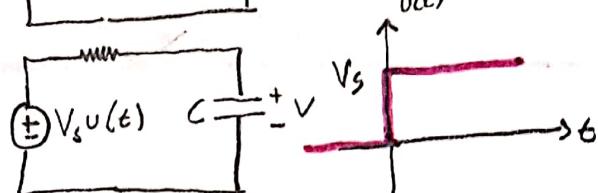

$$V(t) = V_s + (V_0 - V_s) \cdot \exp(-t/\tau), \quad t > 0$$




↳ birim basamak tepkisi

$$\theta(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s) e^{-t/\tau}, & t > 0 \end{cases}$$

$$V_0 = 0$$

$$\theta(t) = \begin{cases} 0, & t < 0 \\ V_s (1 - e^{-t/\tau}), & t > 0 \end{cases}$$
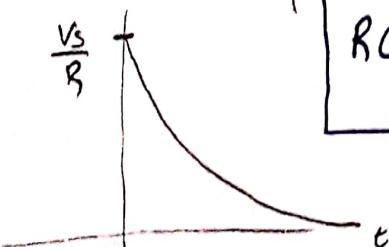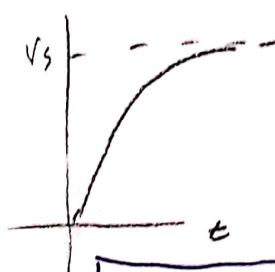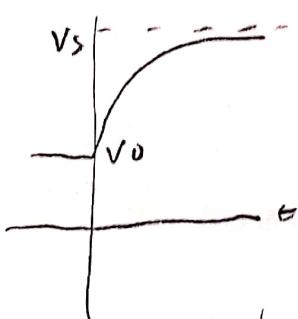
$$\theta(t) = V_s \cdot (1 - \exp(-t/\tau)) \cdot u(t)$$




RC devrenin basamak tepkisi

Sistemin Tcm tepkisi = Doğal Tepki + Zorluklu Tepki

$$V = V_n + V_f$$

$$V = V_0 \cdot \exp(-t/\tau) + V_s (1 - \exp(-t/\tau))$$


RL devrenin basamak tepkisi

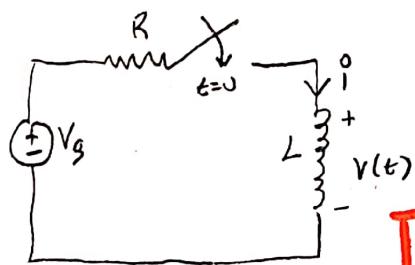

$$i = i_t + i_{ss}$$

$$i(0^-) = i(0^+) = i(0)$$
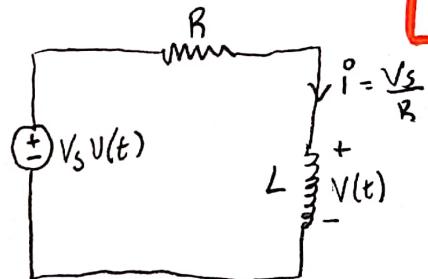
$$\dot{i} = A \exp(-t/\gamma) + \frac{V_s}{R}$$



$$I_0 = A + \frac{V_s}{R} \rightarrow$$




$$A = I_0 - \frac{V_s}{R}$$

$$\gamma = \frac{L}{R}$$

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) \exp(-t/\gamma)$$

$$i(t) = i(\infty) + (i(0) - i(\infty)) \exp(-t/\gamma)$$
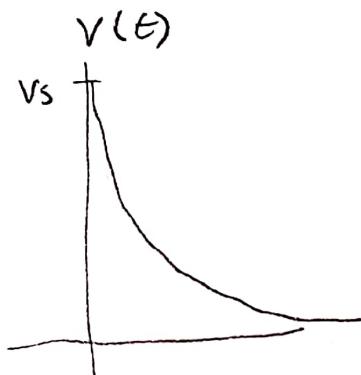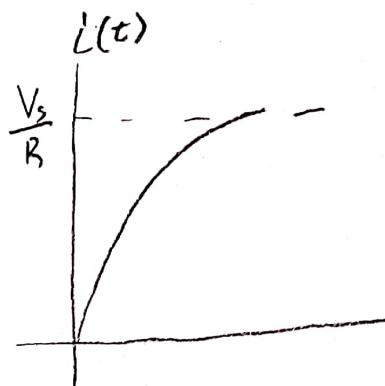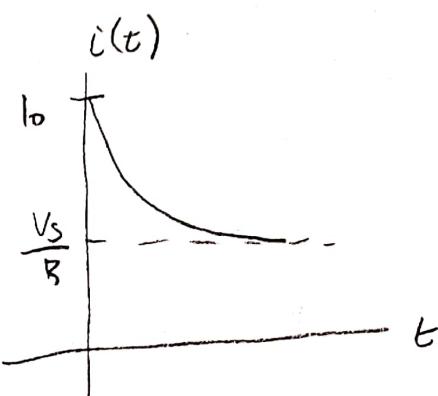
$$i(t) = i(\infty) + (i(t_0) - i(\infty)) \exp(-(t-t_0)/\gamma)$$




$i(0) = 0$ ise

$$i(t) = \frac{V_s}{R} (1 - \exp(-t/\gamma))$$

RL - RC

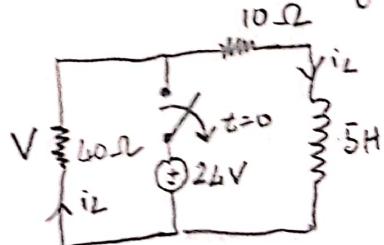Find the labeled voltage at $t=200\text{ms}$



$$i_L(t) = I_0 \cdot \exp(-t/\gamma)$$

$$\gamma = \frac{L}{R}$$

$$V_R(t) = -V_L(t) = R_A \cdot I_0 \cdot \exp(-t/\gamma)$$

$$R_{eq} = 50\Omega$$

$$V_{R_{eq}} + V_L = 0$$

$$i_L = I_0 \cdot \exp(-t/\gamma)$$


$$i_L(0.2) = \frac{12}{25} \cdot \exp(-2)$$

$$\gamma = \frac{5}{50} = 1/10$$

$$V_0 = 24\text{V}$$

$$24 = 50 \cdot I_0 \cdot 1, I_0 = \frac{24}{50}$$
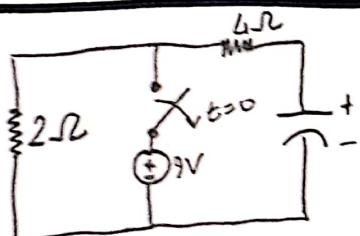
$$\frac{12}{25} \cdot \exp(-2) \cdot 40 = V_{40\Omega}$$



$$V_0 = 9\text{V}$$

$$V_C = V_{R_{eq}} = V(t) = V_0 \cdot \exp(-t/\gamma)$$

$$\gamma = R \cdot C$$


$$t = 200\mu\text{s}$$

$$= 0.0002 \text{ seconds}$$

$$9 \cdot \exp\left(-2 \cdot 10^{-3} / 6 \cdot 10^{-4}\right) \\ = V(0.0002)$$

$$R = 6$$

$$RC = 10^{-4} \cdot 6$$

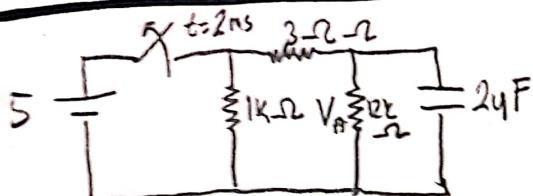

$$V_C = V_A$$

$$V_A = \frac{12}{15} \cdot 5 = 4\text{V} = V_C$$

$$\frac{V_0}{9} \cdot 3^{\frac{t}{2ms}}$$

$$R_{eq} = 3k\Omega$$


$$\gamma = R_{eq} \cdot C = 3k\Omega \cdot 2\mu\text{F} = 6\text{ms}$$

$$V(t) = 5V[1 - u(t-2ms)]$$

$$V_C = V(2\text{ms}) \cdot \exp(-(t-2\text{ms})/\gamma)$$


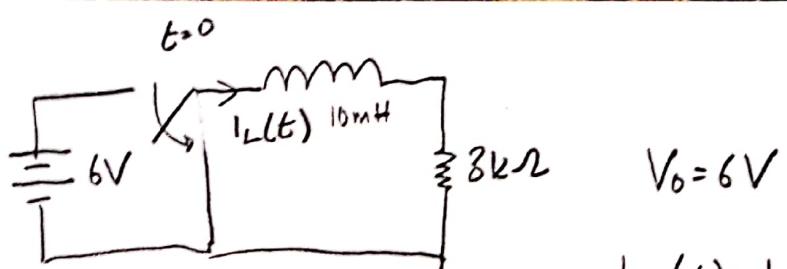
$$V_C = 4V \cdot \exp(-(t-2\text{ms})/6\text{ms})$$



$$V_0 = 6V$$

$$\tau = \frac{L}{R} = \frac{10^{-3}H}{8 \cdot 10^3 \Omega} = \frac{1}{8} \cdot 10^{-6}s =$$

$$I_L(t) = I_0 \cdot \exp(-t/\tau)$$


$$I_L = I_{RC}$$

$$I_0 = \frac{6}{8 \cdot 10^3} = 2 \cdot 10^{-3}$$


$$V_L + V_{RC} = 0$$

$$I_L(t) = 2 \cdot 10^{-3} \cdot \exp(-t/1.2 \cdot 10^{-6})$$

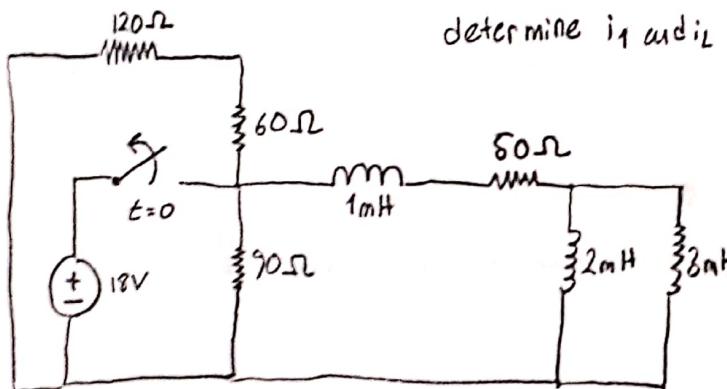
$$V_L(t) = -6V \cdot \exp(-t/1.2 \cdot 10^{-6})$$



↓

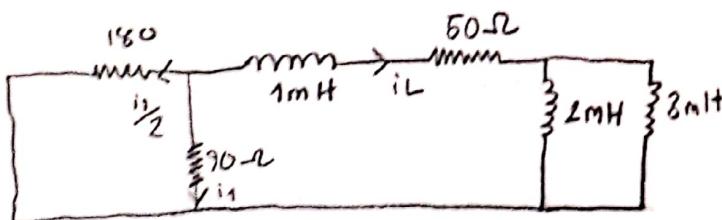


↓

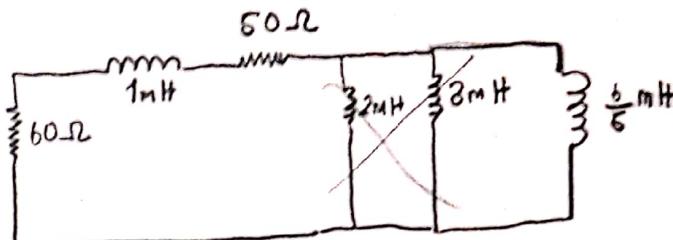


$$V_c(0) = 15V, \quad V_c, V_x, i_x = ?$$

$$\gamma = R \cdot C \text{ sahiye}$$

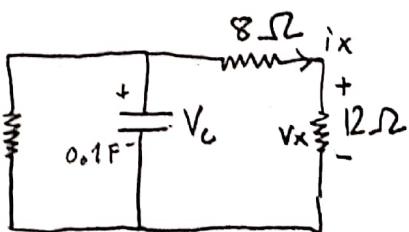

$$V(t) = V_0 \cdot \exp(-t/\gamma)$$

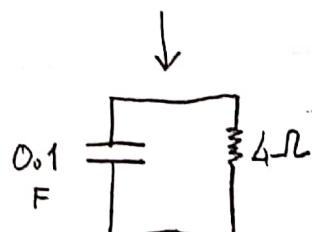

$$\gamma = 0.1 \cdot 4 = 0.4s$$



$$V_c(t) = 15 \cdot \exp(-t/0.4s)$$

$$V_x = V_c \cdot \frac{12}{12+8} = V_c \cdot \frac{3}{5} = 9 \cdot \exp(-t/0.4s)$$

$$i_x = \frac{V_c}{20} = \frac{15}{20} \cdot \exp(-t/0.4s)$$

$$V_c(0) = 60V, \quad V_c(t), V_x, i_o \text{ for } t \geq 0$$

$$\gamma = R \cdot C = 4sn$$

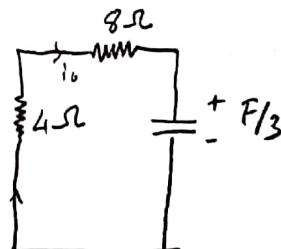
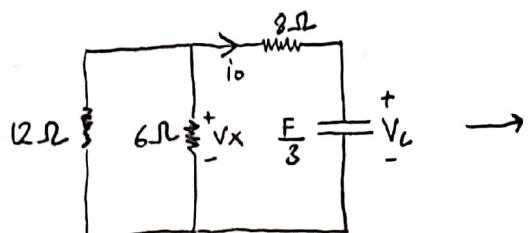


$$V_c(t) = 60 \cdot \exp(-t/4sn) V$$



$$V_x = V_c \cdot \frac{4}{4+8} = 20 \cdot \exp(-t/4sn) V$$

$$i_o(t) = 5 \cdot \exp(-t/4sn) V$$

$$\downarrow \\ 4 \cdot i_o = V_x$$

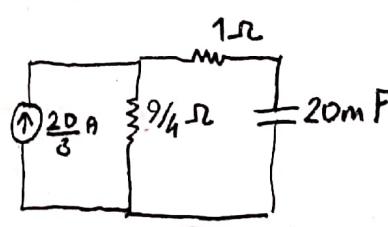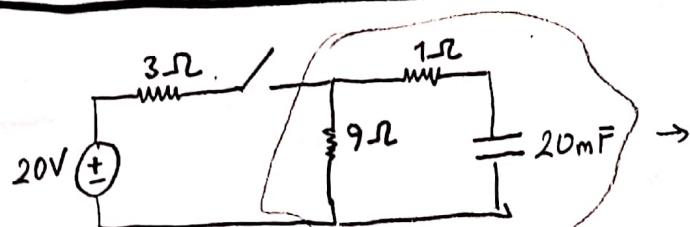

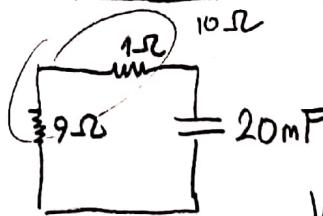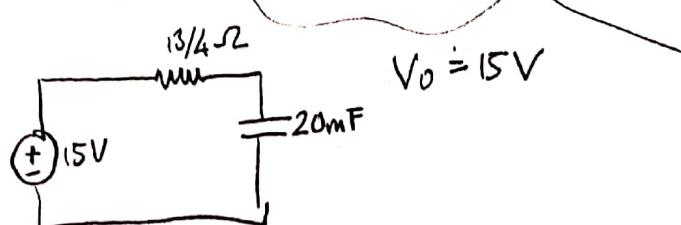
$$\gamma = 2 \cdot 10^{-2} \cdot 10 = 0.2$$



$$V(t) = 15 \exp(-t/0.2sn) V$$

$$E = \frac{1}{2} CV^2$$

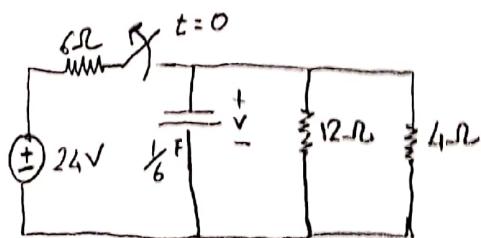


$$V_0 = \frac{24}{9}, 3 = 8V$$

$$V_c(t), E(t) = ?$$

$$\tau = RC = 3 \cdot \frac{1}{6} = \frac{1}{2} \text{ s}$$

$$V_c(t) = 8V \cdot \exp(-t/0.5\text{s})$$

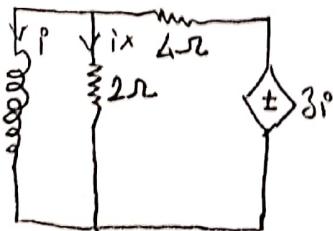
$$E(t) = \frac{1}{2} CV^2 = \frac{1}{2} \frac{1}{6} \cdot 64 = 16/3 \text{ J}$$




$$I_0 = 10A, i(t) = ? \rightarrow t > 0$$

$$\tau = L/R$$

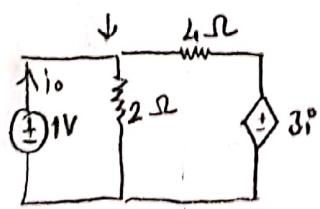
$$i(t) = I_0 \cdot \exp(-t/\tau) = 10 \cdot \exp(-t/(3/2)\text{s})$$



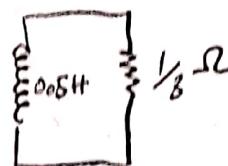
$$R_{TH} = \frac{1V}{I_0} = \frac{1}{3}$$




$$\tau = 3/2 \text{ s}$$

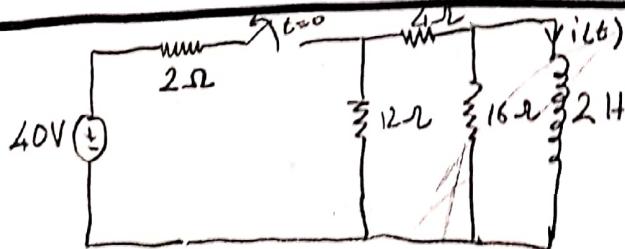

KK


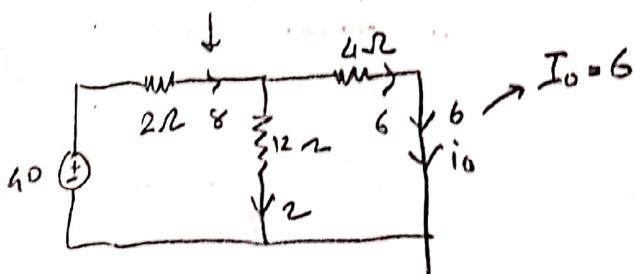


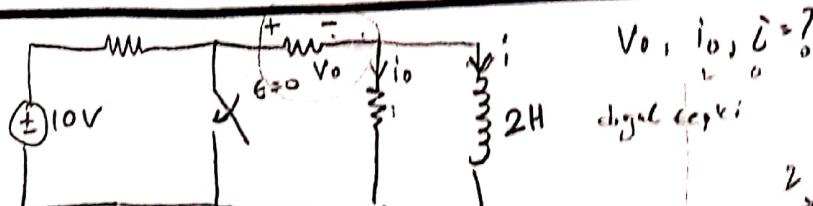
$$I_c(t) = I_0 \cdot \exp(-t/\tau) = 6 \cdot \exp(-t/(1/6)\text{s})$$



digel depri

652

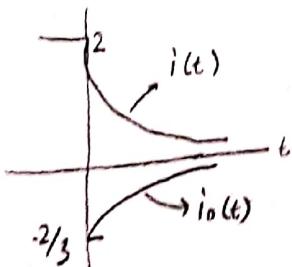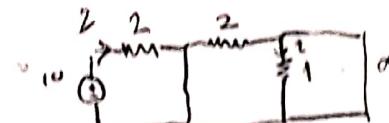

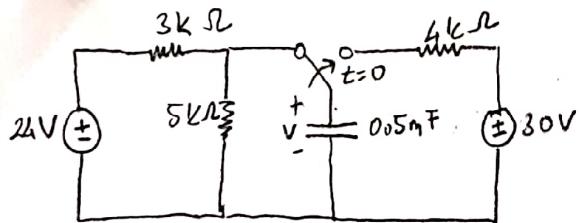


$$\chi = RC = 4k\Omega \cdot 0.5mF = 2s$$

$$V(0^-) = 15V$$

$$V(\infty) = 30V$$

$$V(t) = V(\infty) + [V(0) - V(\infty)] \cdot \exp(-t/\chi)$$
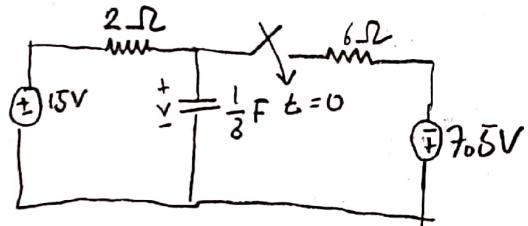
$$V(t) = 30 + (-15) \cdot \exp(-t/2s) \rightarrow t > 0$$



$$V(t), t > 0 ?$$

$$V(0) = 15V$$

$$V(\infty) = 9.375V$$


$$V_{TH} = 3/2$$

$$\chi = 3/2 \cdot 1/8 = 0.375s$$

$$\rightarrow V(t) = V(\infty) + (V(0) - V(\infty)) \exp(-t/\chi)$$

$$= V(t) = 9.375 + (8.625) \cdot \exp(-t/0.375) \quad \frac{1}{8} \cdot \frac{1}{12} = 5 - \frac{7.5}{6} = 6.25$$

$$6.25 \cdot \frac{12}{8} = 9.375$$

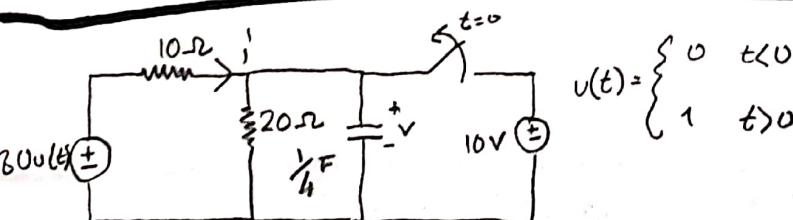

Kondensator übereinstimmen genau

$$atim = C \cdot \frac{dV}{dt} / \frac{V(t)}{Req}$$

$$V(0) = 10V$$

$$t < 0 \text{ ikon } 30u(t) = 0V \\ VEP = -1A$$

$$\begin{array}{c} \uparrow \\ 3 \\ \uparrow \end{array} \quad \begin{array}{c} 1 \\ 10 \\ \uparrow \end{array} \quad \begin{array}{c} 1 \\ 20 \\ \uparrow \end{array}$$

$$\begin{array}{c} \uparrow \\ 3 \\ \uparrow \end{array} \quad \begin{array}{c} 200 \\ \uparrow \\ 80 \end{array}$$

$$\begin{array}{c} \uparrow \\ 20 \\ \uparrow \\ 20 \end{array} \quad \begin{array}{c} 20/3 \\ \uparrow \\ 20 \end{array}$$

$$V(\infty) = 20V \quad t > 0 \text{ ikon } 30u(t) = 20V$$


$$\chi = RC = \frac{20}{8} \cdot \frac{1}{4} = \frac{5}{8}s$$

$$V(t) = 20V - 10 \cdot \exp(-3t/5)V$$

$$i = \frac{V}{20} + C \cdot \frac{dV}{dt} = 1 - 0.5e^{-0.6t} + 3/2 \exp(-0.6t)$$

$$V(t) = \begin{cases} 10V, & t < 0 \\ 20 - 10 \exp(-0.6t), & t > 0 \end{cases}$$
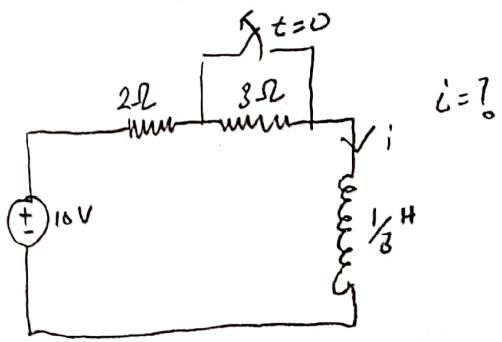
$$i(t) = \begin{cases} -1A, & t < 0 \\ 1 + \exp(-0.6t), & t > 0 \end{cases}$$



$$i(0) = \frac{10}{2} = 5$$


$$i(\infty) = \frac{10}{5} = 2$$

$$R_{TH} = 5\Omega \quad Z = 1/15 \text{ s}n$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/Z}$$

$$i(t) = 2 + 3 \cdot \exp(-15tn) \text{ A} \quad t > 0$$

$$i(t) = 5 \text{ A} \quad t < 0$$

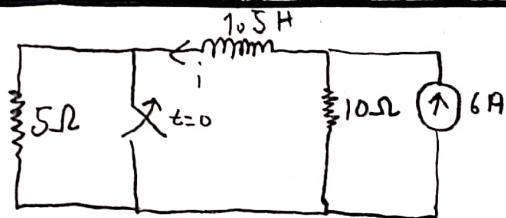


$t < 0$ için 10Ω ve 5Ω kisa devre

$$i(0) = 6 \text{ A}$$

$$i(\infty) = 4 \text{ A}$$

$$R_{EQ} = 15 \Omega \quad \gamma = \frac{1}{10} \text{ s}n$$

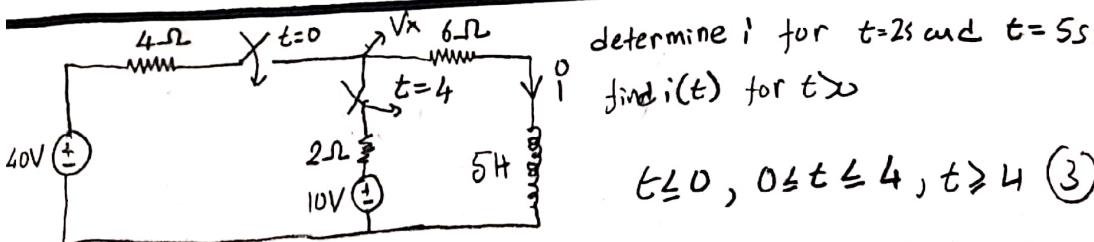
$$i(t) = \begin{cases} 6 \text{ A}, & t \leq 0 \\ 4 + 2 \exp(-10t) \text{ A}, & t > 0 \end{cases}$$



determine i for $t=2s$ and $t=5s$
find $i(t)$ for $t > 0$

$$t \leq 0, 0 \leq t \leq 4, t \geq 4 \quad (3)$$

$$i(0) = 0 \text{ A}$$

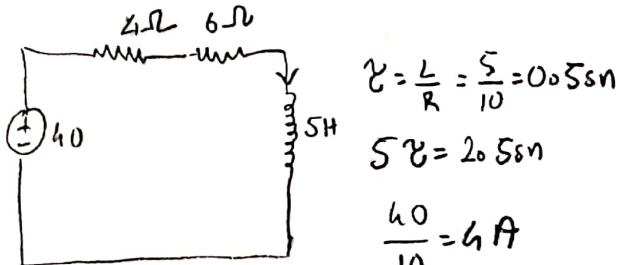

$$i(0) = 0 \text{ A}$$

$$i(\infty) = 4 \text{ A}$$

$$i(t) = 4(1 - \exp(-2t)) \text{ A} \rightarrow 0 \leq t \leq 4$$

$$i(4) = 4 \cdot (1 - e^{-8}) \approx 4 \text{ A}$$

$$i(\infty) = 30/11 \text{ A}$$


$$i(t) = \frac{30}{11} + \frac{14}{11} \exp(-(t-4)/\gamma) \text{ A}$$

$$\frac{Vx-40}{4} + \frac{Vx-10}{2} + \frac{Vx}{6} = 0$$

$$Vx = \frac{180}{11}, \quad i(\infty) = \frac{180}{11} \cdot \frac{1}{6} = \frac{30}{11} \text{ A}$$


$\hookrightarrow t > 4$

RLC

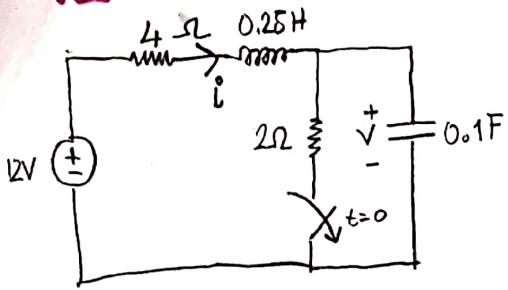


$$i(0), i(\infty), \frac{di(0)}{dt}$$

$$V(0), V(\infty), \frac{dV(0)}{dt}$$

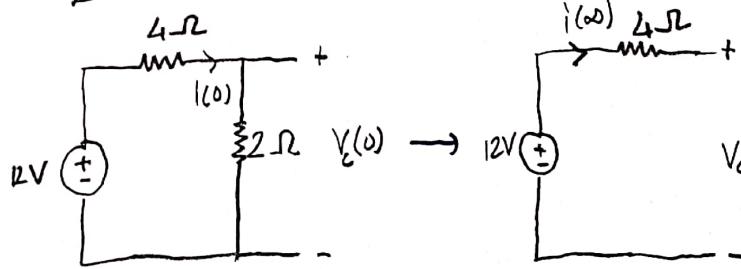

$$V_C(0) \rightarrow 12V$$

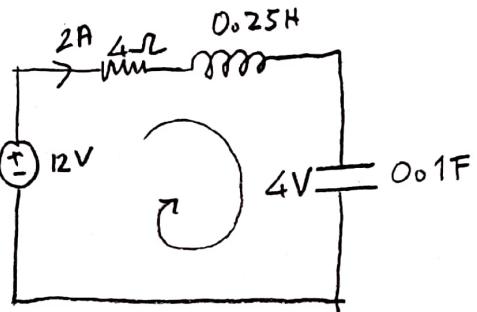

$$\bullet i(0) = 12/6 = 2A$$

$$\bullet i(\infty) = 0A$$


$$\bullet i_C = C \cdot \frac{dV_C}{dt} \rightarrow \frac{dV_C(0)}{dt} = \frac{i_C(0)}{C} = \frac{2A}{0.1F} = 20V/S$$

$$\bullet V_C(0) = 2 \cdot 2 = 4V$$


$$\bullet V_C(\infty) = 12V$$

$$\bullet -12V + 8V + V_L(0) + 4V = 0 \rightarrow V_L(0) = 0$$
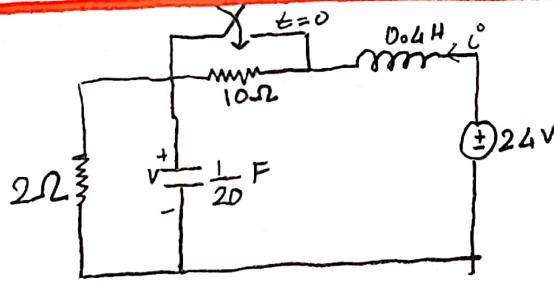
$$V_L = L \cdot \frac{di_L}{dt} \rightarrow \frac{dV_L(0)}{dt} = \frac{V_L(0)}{L} = \frac{0V}{0.25F} = 0A/S$$



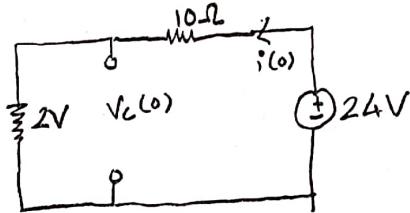
$$i(0), i(\infty), V(0), V(\infty), \frac{di(0)}{dt}, \frac{dV(0)}{dt}$$




$$\bullet i(0) = 24/12 = 2A$$

$$\bullet V_C(0) = 2 \cdot 2 = 4V$$

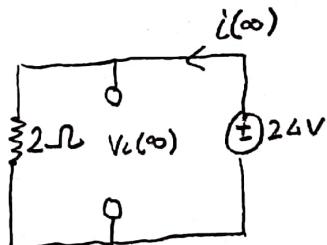

$$\bullet i(\infty) = 24/2 = 12A$$

$$\bullet V(\infty) = 12 \cdot 2 = 24V$$

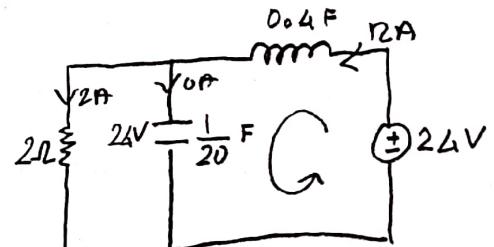


$$\bullet i_C^{(0)} = C \cdot \frac{dV_C^{(0)}}{dt} \rightarrow \frac{i_C^{(0)}}{C} = \frac{dV_C^{(0)}}{dt} = \frac{0V}{1/20} = 0V/S$$


$$\bullet -24V + V_L + 4 = 0 \rightarrow V_L = 20V$$

$$V_L = L \cdot \frac{di_L}{dt} \rightarrow \frac{V_L(0)}{L} = \frac{dV_L(0)}{dt}$$


$$= \frac{20}{0.4} = 50A/S$$

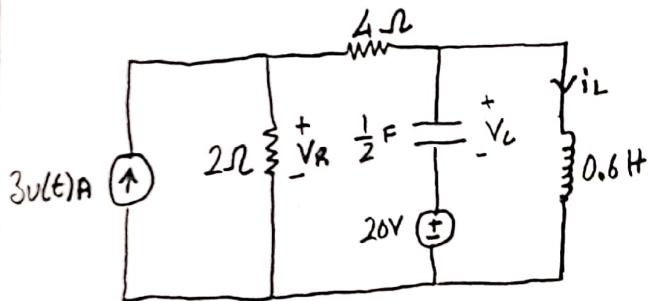

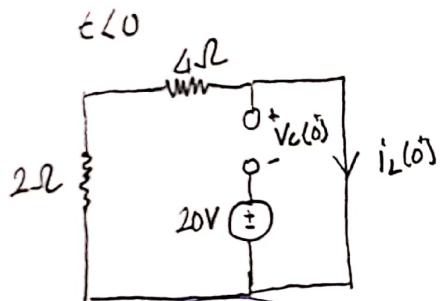$i_L(0^+), V_C(0^+), V_R(0^+)$
 $\frac{di_L(0^+)}{dt}, \frac{dV_C(0^+)}{dt}, \frac{dV_R(0^+)}{dt}$
 $i_L(\infty), V_C(\infty), V_R(\infty)$



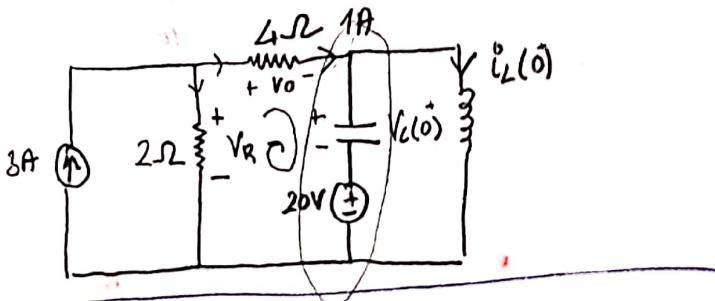- $i_L(0^+) = 0 \text{ A}$
- $V_R(0^+) = -20 \text{ V}$
- $V_C(0^+) = 0 \text{ V}$



$$Z = \frac{V_R}{2} + \frac{V_0}{4} \quad | \quad -V_R + V_0 + V_C(0^+) + 20V = 0$$

$$V_0 = V_R$$

$$\rightarrow V_R(0^+) = V_0(0^+) = \Delta V$$

$$V_L = L \cdot \frac{di_L}{dt} \rightarrow \frac{di_L}{dt} = \frac{V_L}{L} = \frac{V_C(0^+) + 20V}{L} = \frac{0V}{L} = 0 \text{ A/s} \cancel{\Delta}$$

$$i_C = C \cdot \frac{dV_C}{dt} \rightarrow \frac{dV_C}{dt} = \frac{i_C}{C} = \frac{1A}{\frac{1}{2}F} = 2 \text{ V/s} \cancel{\Delta}$$

$$Z = \frac{V_R}{2} + \frac{V_0}{4} \rightarrow 12 = 2V_R + V_0 \rightarrow 0 = 2 \frac{dV_R}{dt} + \frac{dV_0}{dt} \rightarrow 2$$

$$-V_R + V_0 + V_C + 20 = 0 \rightarrow -\frac{dV_R}{dt} + \frac{dV_0}{dt} + \frac{dV_C}{dt} = 0$$

$$-\frac{dV_R}{dt} + \frac{dV_0}{dt} = -2$$


$$\frac{dV_R}{dt} + \frac{dV_0}{dt} = 0 \rightarrow \boxed{\frac{dV_R}{dt} = 2/3}$$

$$V_C(\infty) = -20 \text{ V}$$

$$i_L(\infty) = 3 \cdot \frac{2}{6} = 1 \text{ A}$$

$$V_R(\infty) = 2 \cdot 2 = 4 \text{ V}$$

Seri RLC (Doğal Tepki)

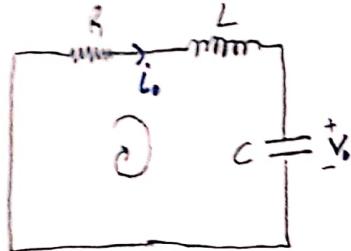

$$\bullet V(0) = V_0 = \frac{1}{C} \cdot \int_{-\infty}^0 i(t) dt$$

$$\bullet i(0) = \dot{i}_0$$

$$\bullet R\dot{i} + L \cdot \frac{di}{dt} + \frac{1}{C} \cdot \int_{-\infty}^0 i(t) dt = 0$$

$$\hookrightarrow t=0 \rightarrow R \cdot i(0) + L \cdot \frac{di(0)}{dt} + \frac{1}{C} \cdot \int_{-\infty}^0 i(t) dt = 0$$

$$\hookrightarrow \frac{di(0)}{dt} = -\frac{1}{L} \cdot (R \cdot i_0 + V_0)$$

$$\bullet R\dot{i} + L \cdot \frac{di}{dt} + \frac{1}{C} \cdot \int_{-\infty}^t i(t) dt = 0 \rightarrow R \cdot \frac{di}{dt} + L \cdot \frac{d^2i}{dt^2} + \frac{i(t)}{C}$$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \cdot \frac{di}{dt} + \frac{1}{LC} = 0 \quad i(t) = A \cdot e^{\delta t}, \quad A \neq 0$$

$$A \cdot s^2 \cdot \exp(st) + \frac{A \cdot R \cdot s}{L} \cdot \exp(st) + \frac{A \cdot \exp(st)}{LC} = 0 \rightarrow A \cdot \exp(st) \left(s^2 + \frac{R}{L} \cdot s + \frac{1}{LC} \right) = 0$$

$$\rightarrow \delta^2 + \frac{R}{L} \cdot s + \frac{1}{LC} = 0, \quad s_{1,2} = \frac{-b \pm \sqrt{\Delta}}{2a}, \quad \Delta = b^2 - 4ac$$

$$\rightarrow s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}, \quad s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

öbümlme faktörü $\frac{R}{2L} = \alpha$, rezonans frekansı $\frac{1}{\sqrt{LC}} = \omega_0$

$$\rightarrow s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \rightarrow \text{doğal frekans}$$

$$i(t) = A \cdot e^{\delta t}$$

$$\rightarrow s^2 + 2\alpha s + \omega_0^2 = 0 \star \rightarrow i(t) = A_1 \cdot e^{s_1 t} + A_2 \cdot e^{s_2 t}$$

$$\rightarrow i(t) = A \cdot e^{st} \rightarrow i(0), \frac{di(0)}{dt}$$

$$i(t) = A_1 \cdot \exp(s_1 \cdot t) + A_2 \cdot \exp(s_2 \cdot t)$$

$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\left. \begin{array}{l} \alpha > \omega_0 \rightarrow \text{asırı sönümlü devre} \\ \alpha = \omega_0 \rightarrow \text{kritik sönümlik} \\ \alpha < \omega_0 \rightarrow \text{eksoili sönümlik} \end{array} \right\}$$


Asırı Sönümlik / Overdamped

$\alpha > \omega_0$

$$i(t) = A_1 \cdot \exp(s_1 t) + A_2 \cdot \exp(s_2 t)$$

$$C) \frac{4L}{R^2} \text{ iken}$$
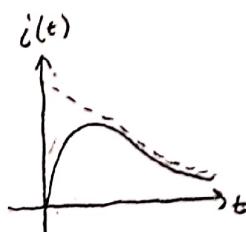
$$\lim_{t \rightarrow \infty} i(t) = 0 \text{ olur.}$$



Kritik Sönümlik / Critically Damped

$$\alpha = \omega_0$$

$$\left. \begin{array}{l} s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \end{array} \right\} s_1 = s_2 = -\alpha$$

$$i(t) = A_1 \exp(-\alpha t) + A_2 \cdot \exp(-\alpha t) = A_3 \exp(-\alpha t) \times$$


$$\frac{d^2i}{dt^2} + 2\alpha \frac{di}{dt} + \alpha^2 i = 0 \rightarrow \frac{d}{dt} \left(\frac{di}{dt} + \alpha i \right) + \alpha \left(\frac{di}{dt} + \alpha i \right) = 0$$

$$\frac{dt}{dt} + q \cdot f = 0 \rightarrow f = A_1 \cdot \exp(-\alpha t) = \frac{di}{dt} + \alpha i$$

$$\frac{di}{dt} + \alpha i = A_1 \cdot \exp(-\alpha t) \rightarrow \exp(\alpha t) \frac{di}{dt} + \exp(\alpha t) \cdot \alpha \cdot i = A_1$$

$$\frac{d}{dt} (\exp(\alpha t) \cdot i) = A_1 \rightarrow \exp(\alpha t) \cdot i = A_1 t + A_2$$
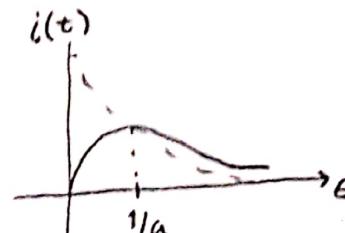
$$i = (A_1 t + A_2) \cdot \exp(-\alpha t)$$



Eksili Sönmeli


$\alpha < \omega_0$


$$\begin{aligned} S_1 &= -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} = S_1 = -\alpha + j\omega_d \quad \rightarrow \quad j = \sqrt{-1} \\ S_2 &= -\alpha - \sqrt{-(\omega_0^2 - \alpha^2)} = S_2 = -\alpha + j\omega_d \quad \rightarrow \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2} \\ &\qquad\qquad\qquad \hookrightarrow \text{sönmelme frekansı} \end{aligned}$$

$$\begin{aligned} i(t) &= A_1 \cdot \exp(-[\alpha - j\omega_d] \cdot t) + A_2 \cdot \exp(-[\alpha + j\omega_d] \cdot t) \\ &= \exp(-\alpha t) \left(A_1 \cdot \exp(j\omega_d \cdot t) + A_2 \cdot \exp(-j\omega_d \cdot t) \right) \end{aligned}$$

$$\hookrightarrow e^{j\theta} = \cos \theta + j \sin \theta / e^{-j\theta} = \cos \theta - j \sin \theta$$
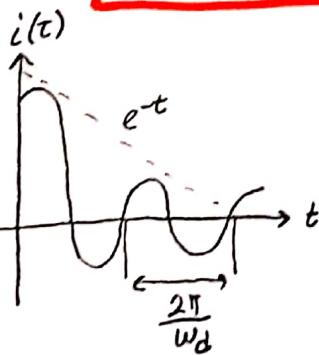
$$\begin{aligned} i(t) &= \exp(-\alpha t) \left[A_1 (\cos \omega_d t + j \sin \omega_d t) + A_2 (\cos \omega_d t - j \sin \omega_d t) \right] \\ &= \exp(-\alpha t) \left[(A_1 + A_2) \cos \omega_d t + j(A_1 - A_2) \sin \omega_d t \right] \\ &= \boxed{\exp(-\alpha t) \left[B_1 \cos \omega_d t + j B_2 \sin \omega_d t \right]} \end{aligned}$$



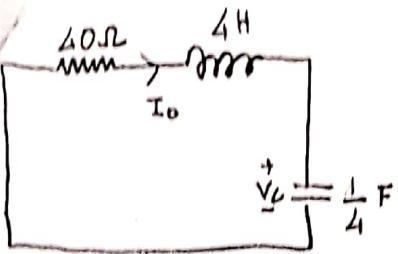

$$\alpha = \frac{R}{2L} = \frac{40}{8} = 5 \quad \alpha > \omega_0 \text{ Ağırlı dönmeli}$$

$$s^2 + 2\alpha s + \omega_0^2$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1$$


$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_{1/2} = -5 \pm \sqrt{24} \quad \begin{cases} s_1 = -0.101 \\ s_2 = -9.899 \end{cases}$$

$$R=5, L=5H, C=2mF, \alpha=? , \omega_0=? , s_1=? , s_2=?$$

$$\alpha = \frac{R}{2L} = 1, \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5.2/1000}} = 10 \quad \alpha < \omega_0 \rightarrow \text{Kritik sonumlu}$$

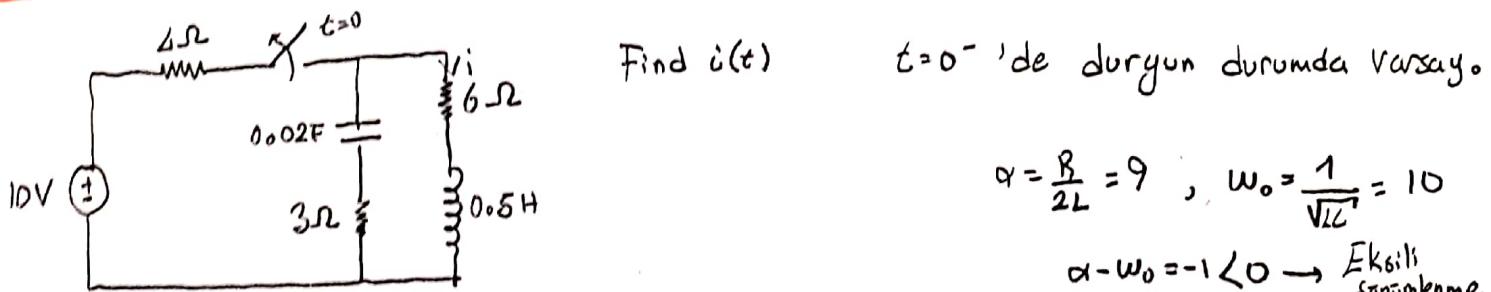
$$s_{1/2} = -1 \pm \sqrt{-99} \quad \begin{cases} s_1 = -1 + j\sqrt{99} \\ s_2 = -1 - j\sqrt{99} \end{cases}$$



$$\alpha = \frac{R}{2L} = 9, \omega_0 = \frac{1}{\sqrt{LC}} = 10$$

$\alpha - \omega_0 = -1 < 0 \rightarrow \text{Eksiksiz sonumlanma}$
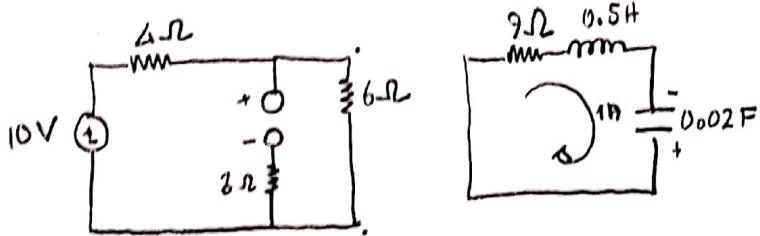
$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$



$$\bullet V_C(0) > 6 \times 1 = 6V$$

$$9 + V_L - 6V = 0 \rightarrow V_L = -3V$$

$$\left[\frac{di(0)}{dt} = \frac{V_L}{L} = \frac{-3}{0.5} = -6 \text{ A/s} \right]$$

$$\bullet i(0) = 10/10 = 1A$$


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{100 - 81} = \sqrt{19} \approx 4.359 \rightarrow i(t) = e^{-9t} (B_1 \cos(4.359t) + B_2 \sin(4.359t))$$

$$i(0) = B_1 = 1$$

$$\frac{di(0)}{dt} = -9e^{-9t} [B_1 \cos(4.359t) + B_2 \sin(4.359t)] + e^{-9t} [-B_1(4.359) \cdot \sin(4.359t) + B_2(4.359) \cdot \cos(4.359t)]$$

$$\frac{di(0)}{dt} = -9B_1 + B_2 \cdot 4.359 = -6 \rightarrow B_2 = 0.6882 \quad \checkmark \checkmark$$

Paralel RLC (Doğal Tepki)

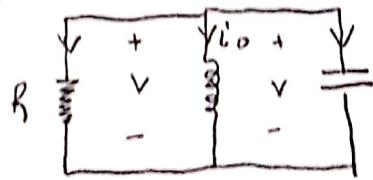

$$i_L(0) = I_0 = \frac{1}{L} \cdot \int_{-\infty}^0 V(t) dt \quad \left. \begin{array}{l} \\ \end{array} \right\} \frac{V}{R} + \frac{1}{L} \cdot \int_{-\infty}^t V(t) dt + C \cdot \frac{dV}{dt} = 0$$

$$V_C(0) = V_0$$

$$\frac{dV(t)}{dt} = -\frac{V_0}{RC} - \frac{I_0}{C} = -\frac{(I_0 + RI_0)}{RC}$$

$$\boxed{\frac{d^2V}{dt^2} + \frac{1}{RC} \cdot \frac{dV}{dt} + \frac{V}{L} = 0}$$

$$\boxed{\frac{s^2}{RC} + \frac{s}{LC} + \frac{1}{LC} = 0}$$

$$\boxed{s_{1/2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}}$$

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{\omega_0^2}}$$

$$s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{\omega_0^2}}$$

$$\alpha = +\frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\alpha < \omega_0 \longrightarrow V(t) = e^{-\alpha t} \cdot [B_1 \cos \omega_d t + B_2 \sin \omega_d t] \rightarrow \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\boxed{s_{1/2} = -\alpha \pm j\omega_d}$$

$$\alpha = \omega_0 \longrightarrow V(t) = (A_1 + A_2 t) e^{-\alpha t}$$

$$\alpha > \omega_0 \longrightarrow V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


find $v(t)$ for $t > 0$

$$V(0) = 5V, i(0) = 0, L = 1H, C = 10mF$$

$$R = 1.923$$

$$\begin{cases} R = 5 \\ R = 6.25 \end{cases}$$

sen 45°

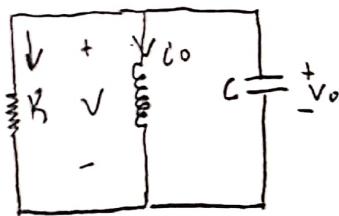

$$\alpha = \frac{1}{2RC} = \frac{1}{2(1.923) \cdot 10^{-2}} = 26$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \cdot 10^{-2}}} = 10$$

$\alpha > \omega_0 \rightarrow$ overdamped

$$\delta_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \rightarrow \delta_1 = -2, \delta_2 = -50$$

$$v(t) = A_1 e^{\delta_1 t} + A_2 e^{\delta_2 t} = A_1 e^{-2t} + A_2 e^{-50t}$$


$$v(0) = A_1 + A_2 = 5$$

$$\frac{dv(t)}{dt} = -2A_1 e^{-2t} - 50A_2 e^{-50t} \quad \Rightarrow \quad \begin{cases} A_1 = 0.2083 \\ A_2 = 5.2083 \end{cases}$$

$$\frac{dV(0)}{dt} = -2A_1 - 50A_2 = -260$$

$$\frac{dV(0)}{dt} = \frac{(V_0 + RI_0)}{RC} = -260$$

Seri RLC (Basamak Testisi)

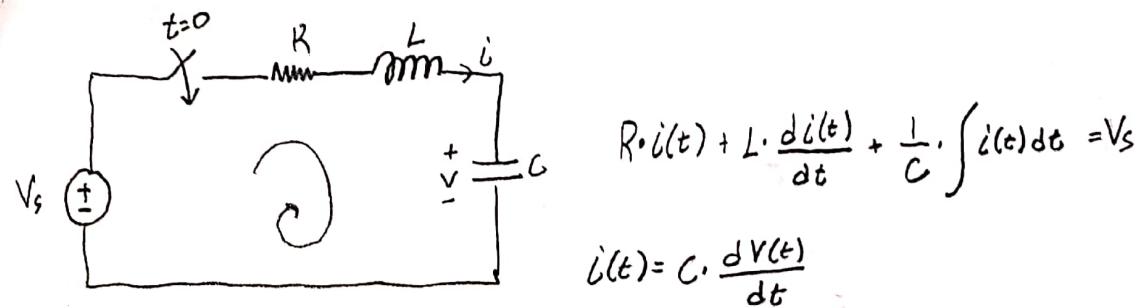

$$R \cdot C \cdot \frac{dV(t)}{dt} + L \cdot C \cdot \frac{d^2V(t)}{dt^2} + V(t) = V_s$$


$$\frac{d^2V(t)}{dt^2} + \frac{R}{L} \cdot \frac{dV(t)}{dt} + \frac{V(t)}{LC} = \frac{V_s}{LC}$$

$$\left[s^2 + \frac{R}{L} \cdot s + \frac{1}{LC} \right] V(t) = \frac{V_s}{LC}$$
$$V(\infty) = V_s$$

$$V(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \rightarrow \text{Overdamped}$$

$$V(t) = V_s + (A_1 + A_2 t) \cdot e^{-\alpha t} \quad \rightarrow \text{Critically Damped}$$
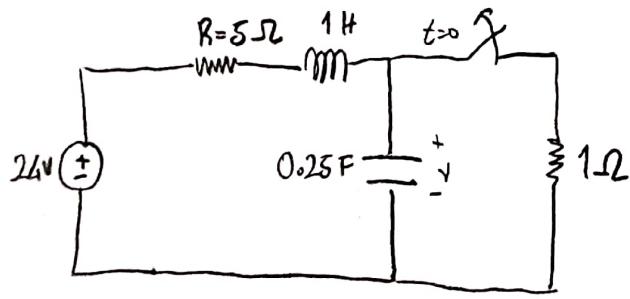
$$V(t) = V_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad \rightarrow \text{Underdamped}$$



$$\alpha = \frac{R}{2L} = \frac{5}{2} = 2.5$$

$$w_0 = \frac{1}{\sqrt{LC}} = 2 \quad \omega_{1/2} = -\alpha \pm \sqrt{\alpha^2 - w_0^2}$$

$$\omega_1 = -1 \quad \omega_2 = -5$$

$$i(0) = 24/6 = 4A$$

$$V(0) = 1.4 = 1.4V$$

$$V(0) = 24V$$

$$V(t) = 24 + A_1 e^{-t} + A_2 e^{-4t}$$

$$V(0) = 24 + A_1 + A_2 = 4V$$

$$i(0) = C \cdot \frac{dV(t)}{dt}$$


$$\frac{dV(t)}{dt} = -A_1 e^{-t} - 4A_2 e^{-4t}$$

$$\frac{dV(0)}{dt} = \frac{i(0)}{C} = \frac{4}{0.025} = 16$$

$$\frac{dV(0)}{dt} = -A_1 - 4A_2 = 16$$

$$A_1 = -64/3$$
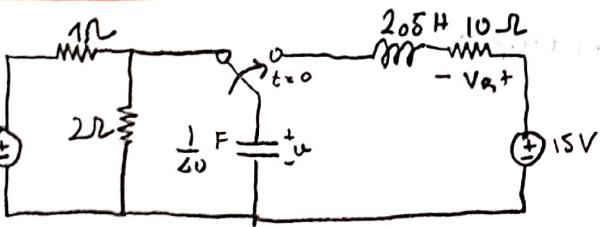
$$A_2 = 4/3 \quad V(t) = 24 + \frac{4}{3} (-16e^{-t} + e^{-4t})V$$



$$V(0) = \frac{18}{8} \cdot 2 = 12V$$

$$i(0) = 0A$$

$$\alpha = \frac{R}{2L} = 2 \quad w_0 = \frac{1}{\sqrt{LC}} = 4 \quad \alpha < w_0 \quad \hookrightarrow \text{Exkssili}$$

$$V(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) + V_S$$

$$V(0) = B_1 + V_S = B_1 + 15$$

$$w_d = \sqrt{w_0^2 - \alpha^2} = \sqrt{16 - 4^2} = \sqrt{12} = 3.46$$


$$B_1 = -3V$$

$$\frac{dV(t)}{dt} = -2e^{-2t} [-3 \cdot \cos(3.46t) + B_2 \cdot \sin(3.46t)] + e^{-2t} [-3 \cdot 3.46 \sin(3.46t) + B_2 \cdot 3.46 \cos(3.46t)]$$

$$\frac{dV(0)}{dt} = -2 \cdot (-3) + B_2 \cdot 3.46 = 0 \rightarrow B_2 = -1.73$$

$$V_R(t) = R \cdot C \cdot \frac{dV(t)}{dt}$$

Paralel RLC (Basamak Tepkisi)

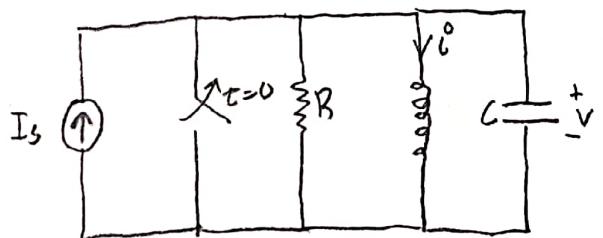

$$\frac{V}{R} + i + C \cdot \frac{dV}{dt} = I_s \quad , \quad V = L \cdot \frac{di}{dt}$$

$$\frac{d^2i}{dt^2} + \frac{1}{RC} \cdot \frac{di}{dt} + \frac{1}{LC} = \frac{I_s}{LC}$$

$$\frac{di(0)}{dt} = \frac{V_0}{V_L} \rightarrow v_L$$


$$i(0)$$

$$i(t) = I_s + A_1 e^{\delta t} + A_2 e^{\delta t} \rightarrow \text{Overdamped}$$

$$\alpha = \frac{1}{2RC}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$i(t) = I_s + (A_1 + A_2 t) e^{-\alpha t} \rightarrow \text{Critically Damped}$$
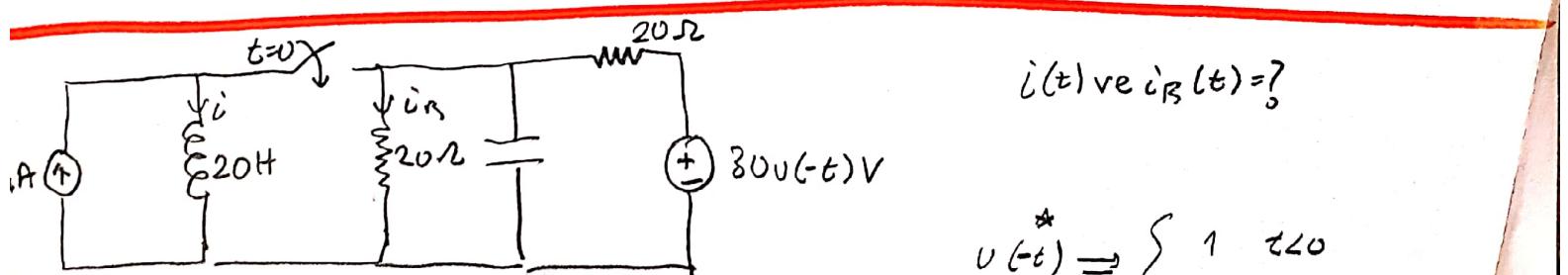
$$i(t) = I_s + (A_1 \cos \omega_0 t + A_2 \sin \omega_0 t) e^{-\alpha t} \rightarrow \text{Underdamped}$$



$$i(t) \text{ ve } i_R(t) = ?$$

$$v(-t)^* \Rightarrow \begin{cases} 1 & t < 0 \\ 0 & t > 0 \end{cases}$$

$$i(0) = 4A$$

$$V(0) = \frac{30}{40} \cdot 20 = 15V$$

$$V_L(0) = \frac{di(0)}{dt} \cdot L \rightarrow \frac{di(0)}{dt} = \frac{15}{20} = 0.75 \text{ A/s}$$

$$\alpha = \frac{1}{2RC} = 6.25, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2.5 \rightarrow 6.25 > 2.5 \rightarrow \text{Overdamped}$$

$$\delta_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \rightarrow \delta_1 = -11.978 \quad \delta_2 = -0.5218$$

$$i(t) = I_s + (A_1 \cdot e^{-11.978t} + A_2 \cdot e^{-0.5218t}) \quad A \quad i(0) = 4 + A_1 + A_2 = 4, \quad A_1 = -A_2$$

$$\frac{di(t)}{dt} = -11.978 A_1 \cdot e^{-11.978t} - 0.5218 A_2 \cdot e^{-0.5218t}$$


$$-11.978 A_1 - 0.5218 A_2 = 0.75$$

$$\frac{di(0)}{dt} = 0.75$$

$$A_2 = 0.0655$$

$$A_1 = -0.0655$$

$$i_R(t) = \frac{V(t)}{R}$$

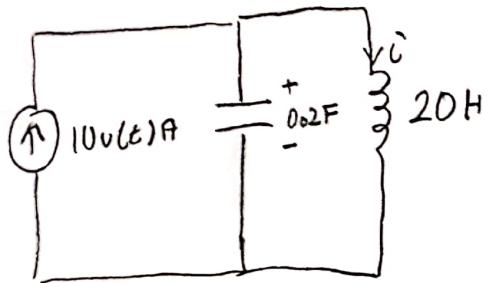

$$L \cdot \frac{dV}{dt} + i = 10 \quad , \quad V = \frac{di}{dt} \cdot L$$

$$C \cdot L \cdot \frac{d^2i}{dt^2} + i = 10$$

$$\frac{d^2i}{dt^2} + \frac{i}{LC} = \frac{10}{LC}$$

$$\alpha = 0$$

$$\omega^2 + \omega_0^2$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \cdot 0.02}} = 0.5$$

$$\omega_d t = \sqrt{\omega_0^2 - \alpha^2} = \omega_0$$


$$i(t) = I_s + e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$i(t) = 10 + B_1 \cos 0.5t + B_2 \sin 0.5t$$

$$i(0) = 10 + B_1 = 0 \rightarrow B_1 = -10$$

$$\frac{di(0)}{dt} = 0 \quad B_2 = 0$$


OPAMP

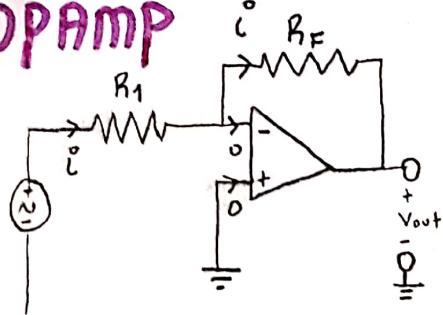

$$i = \frac{V_{in}}{R} = -\frac{V_{out}}{R_f}$$


Ideal

Evren Kuvvetlendinci
Inverting amplifier

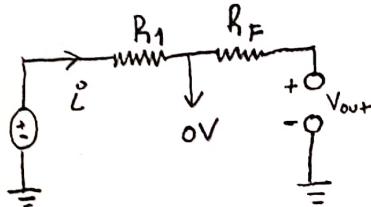

$$V_{out} = -V_{in} \cdot \frac{R_f}{R_1}$$
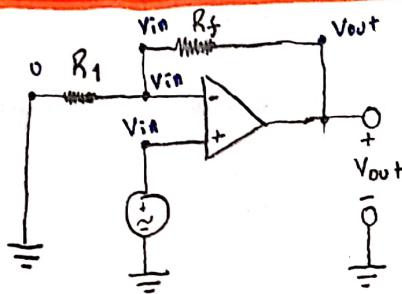
$$\text{Kazanç} = \frac{V_{out}}{V_{in}}$$




$$i_{R_1} + i_{R_f} = 0$$

$$i_{R_1} = \frac{V_{in}}{R_1}, \quad i_{R_f} = \frac{V_{in} - V_{out}}{R_f}$$

$$V_{out} = V_{in} \cdot \left(1 + \frac{R_f}{R_1}\right)$$

Evirmeysen Kuvvetlendinci


non-inverting amplifier

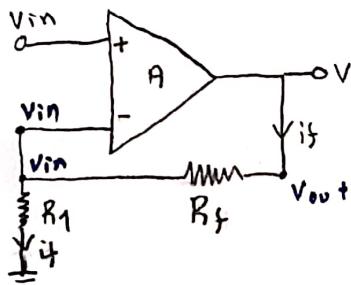

$$i_f = \frac{V_{in} - 0}{R_1} = \frac{V_{out} - V_{in}}{R_f}$$

$$V_{out} = V_{in} \cdot \left(1 + \frac{R_f}{R_1}\right)$$

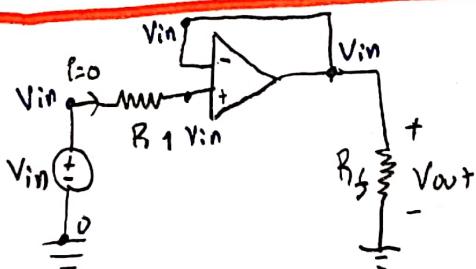
$$\text{Kazanç} = \left(1 + \frac{R_f}{R_1}\right)$$



$$V_{in} = V_{out}$$

Buffer

Voltage Follower

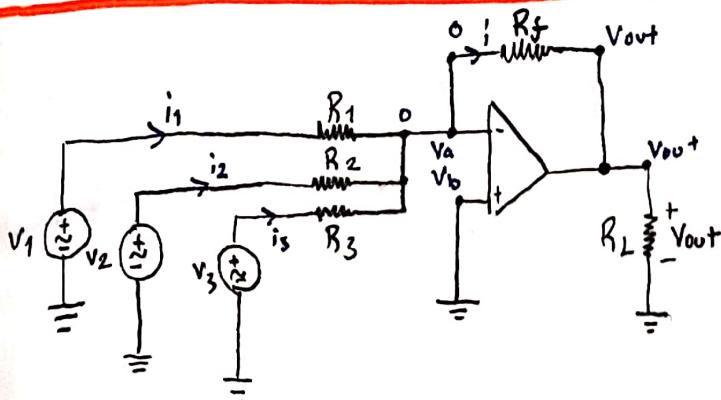


$$V_a = V_b = 0V$$

$$i_1 + i_2 + i_3 = i \rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_{out}}{R_f}$$


$$V_{out} = -R_f \cdot \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

Summing Amplifier

Toplayıcı Yükselticisi

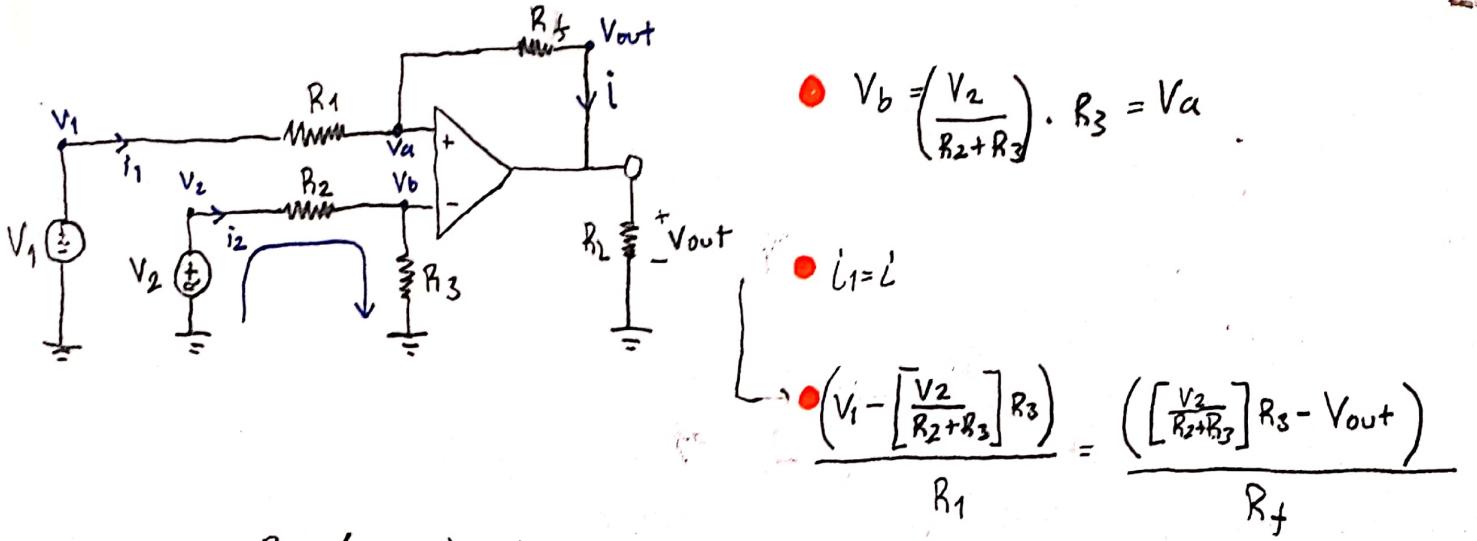

Difference Amplifier

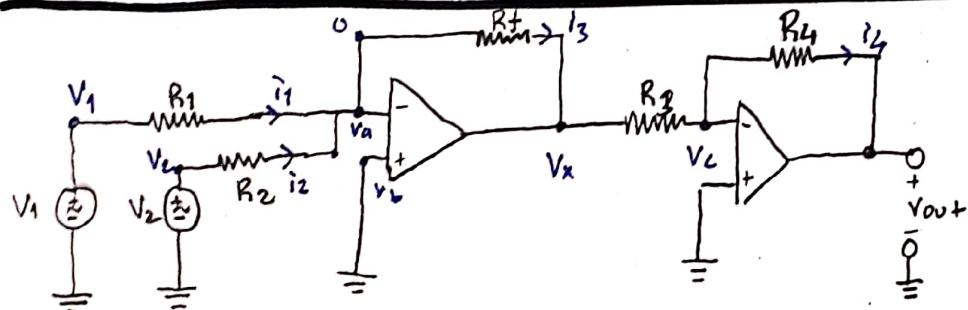


$\bullet i_1 = i_2 = i_3 = i_4, V_a = V_b = V_c = 0$


$\bullet \frac{V_1}{R_1} + \frac{V_2}{R_2} = -\frac{V_x}{R_f} \rightarrow V_x = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$

$\bullet \frac{V_x}{R_3} = -\frac{V_{out+}}{R_4} \rightarrow V_{out+} = \frac{R_4}{R_3} \cdot R_f \cdot \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$


OPAMP

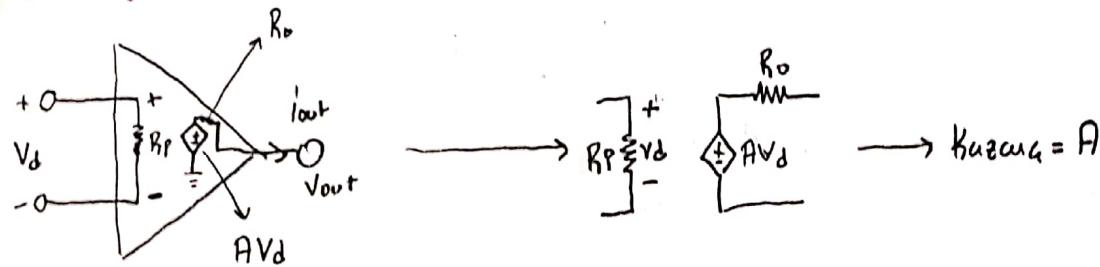

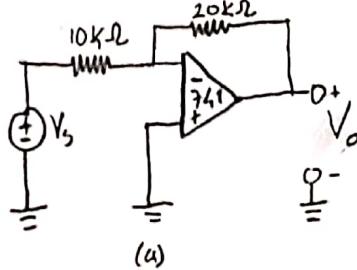A 741 opamp has an open-loop voltage gain of 2×10^5 , input resistance of $2M\Omega$ and input noise of 50nV . The opamp is used in the circuit of
 a. Find the closed-loop gain V_o/V_s , determine current i when $V_s = 2V_o$.



→

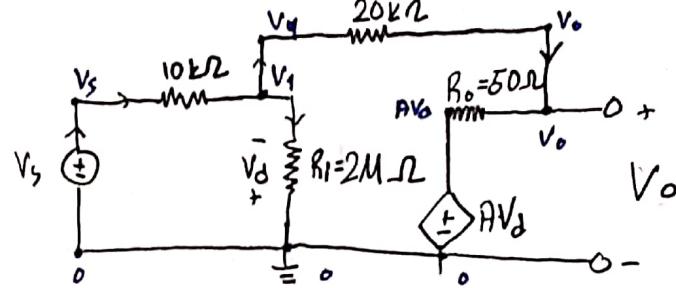

$$A = 2 \times 10^5$$

$$\frac{V_s - V_1}{10k} = \frac{V_1 - V_o}{20k} + \frac{V_1}{2M}$$

$$\frac{V_1 - V_o}{200k} = \frac{V_o - A V_1}{50}$$

↓

$$V_1 - V_o = 400(V_o + A V_1)$$

$$200V_s - 200V_1 = 100V_1 - 100V_o + V_1$$


$$\approx [301V_1 - 200V_s - 100V_o = 0]$$

$$\rightarrow 3V_1 - 2V_s - V_o = 0 \rightarrow V_1 = \frac{2V_s + V_o}{3}$$

$$\frac{V_o}{V_s} \approx -2$$

1. Dereceden OPAMP

integral Alicki Devre

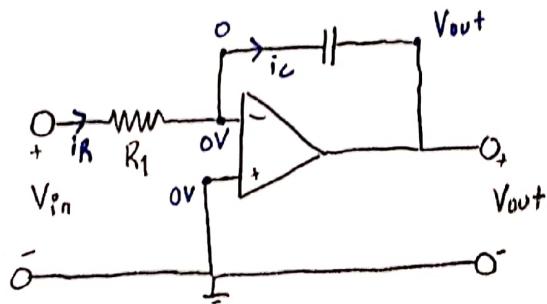


$$i_R = i_C, \quad i_R = \frac{V_{in}}{R_1}, \quad i_C = -C \cdot \frac{dV_{out}}{dt}$$

$$\frac{V_{in}}{R} = -C \cdot \frac{dV_{out}}{dt} \rightarrow dV_{out} = -\frac{1}{RC} \cdot V_{in} dt$$

$$\int dV_{out} = -\frac{1}{RC} \cdot \int_{0}^{t_1} V_{in} dt$$

$$V_{out} = -\frac{1}{RC} \cdot \int_{0}^{t_1} V_{in} dt$$


Türer Alicki Devre

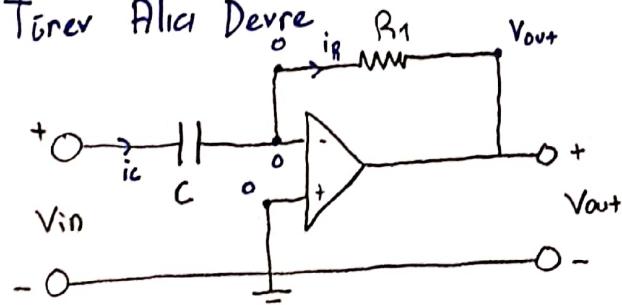

$$i_C = i_R \rightarrow i_R = \frac{-V_{out}}{R_1}, \quad i_C = C \cdot \frac{dV_{in}}{dt}$$

$$C \cdot \frac{dV_{in}}{dt} = \frac{-V_{out}}{R_1} \rightarrow dV_{in} = -\frac{V_{out} dt}{R_1 C}$$
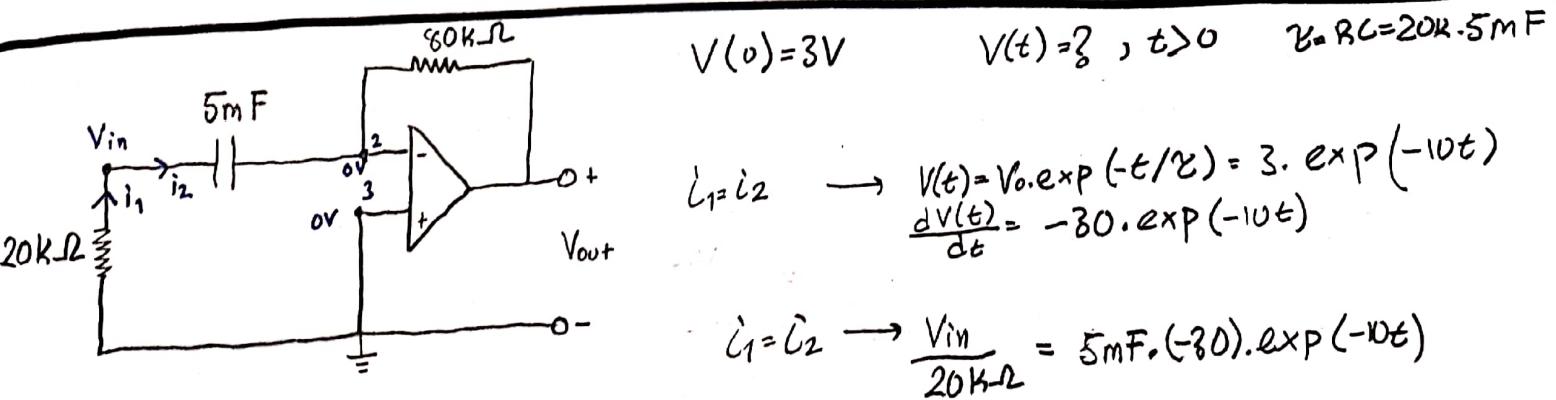
$$V_{out} = -R_1 C \cdot \frac{dV_{in}}{dt}$$



$$V(0) = 3V$$

$$V(t) = ? , t > 0$$

$$\gamma = RC = 20k \cdot 5mF$$


$$i_1 = i_2 \rightarrow V(t) = V_0 \cdot \exp(-t/\gamma) = 3 \cdot \exp(-10t)$$

$$\frac{dV(t)}{dt} = -30 \cdot \exp(-10t)$$

$$i_1 = i_2 \rightarrow \frac{V_{in}}{20k\Omega} = 5mF \cdot (-30) \cdot \exp(-10t)$$

$$V_{out} = -RC \cdot \frac{dV_{in}}{dt} = 12 \cdot \exp(-10t)$$

Sinüzodial Gerilim

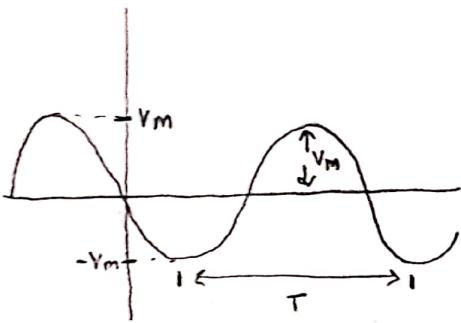

Genlik
 $\bullet V(t) = V_m \cdot \cos(\omega t + \phi) \text{ V}$

$f = \frac{1}{T} (\text{Hz})$

$\omega = 2\pi f = \frac{2\pi}{T} (\text{rad/s})$




$T \rightarrow \text{periyot}$

$\phi \rightarrow \text{faz}$



$\bullet V_{rms} = \sqrt{\frac{1}{T} \cdot \int_{t_0}^{t_0+T} V_m^2 \cdot \cos^2(\omega t + \phi) dt}, \quad \bullet V_{rms} = \frac{V_m}{\sqrt{2}}$

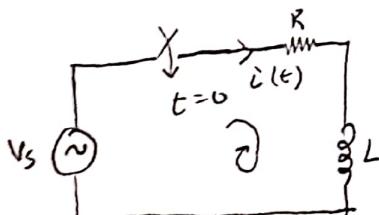$V(t) = 100 \cdot \cos(2\pi \cdot 50t + 50) \text{ V}$
 galilik → faz
 ↓
 frekans



$\bullet L \cdot \frac{di}{dt} + R \cdot i = V_m \cos(\omega t + \phi)$

$V_s = V_m \cdot \cos(\omega t + \phi)$

$\bullet i = \underbrace{\frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta)}_{\text{dogal (geçici)}} \underbrace{e^{-(R/L)t}}_{\text{Kücük (zorlanma)}} + \underbrace{\frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cdot \cos(\omega t + \phi - \theta)}_{\text{Küçük (zorlanma)}}$

$i(t) = i_e(t) + i_{ss}(t)$

Fazörler

Fazör, bir sinyoidalın genlik ve faz bilgisini taşıyan karmaşık sayı.

- $e^{j\theta} = \cos\theta + j\sin\theta$
 - $\operatorname{Re}\{e^{j\theta}\} = \cos\theta$
 - $\operatorname{Im}\{e^{j\theta}\} = \sin\theta$
- $V = V_m \cdot \cos(\omega t + \phi)$
 $= V_m \cdot \operatorname{Re}(e^{j(\omega t + \phi)}) = V_m \cdot \operatorname{Re}(e^{j\omega t} \cdot e^{j\phi}) = \operatorname{Re}(V_m \cdot e^{j\phi} \cdot e^{j\omega t})$
 - ↑ faz
 - ↓ frekans
 - genlik
- $\bar{V} = V_m \cdot e^{j\phi} = P\{V_m \cdot \cos(\omega t + \phi)\}$
 - ↳ fazör gösterim
- $\bar{V} = V_m \cdot e^{j\phi} = V_m \cdot \cos\phi + j \cdot V_m \cdot \sin\phi$
 $V_m \cdot e^{j\phi} = V_m \cdot \underline{\angle \phi}$
 - ↳ polar gösterim

Ters Fazör Dönüşümü

$$V_m \cdot e^{j\phi} \xrightarrow{P^{-1}} V_m \cdot \cos(\omega t + \phi)$$

$$1) V_m \cdot e^{j\phi} \times e^{j\omega t}$$

$$2) \operatorname{Re}\{V_m \cdot e^{j\phi} \times e^{j\omega t}\}$$

Kalıcı durum tepkisi $\operatorname{Re}\{A \cdot e^{j\beta} \cdot e^{j\omega t}\}$

$$i_{ss}(t) = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cdot \cos(\omega t + \underbrace{\phi - \theta}_{\beta})$$

$$L \cdot \frac{di}{dt} + R \cdot i = V_m \cdot \cos(\omega t + \phi), \quad i_{ss}(t) = \operatorname{Re}\{I_m \cdot e^{j\beta} \cdot e^{j\omega t}\}$$

$$\Rightarrow \operatorname{Re}\{j\omega L e^{j\beta} \cdot e^{j\omega t}\} + \operatorname{Re}\{R \cdot I_m \cdot e^{j\beta} \cdot e^{j\omega t}\} = \operatorname{Re}\{V_m \cdot e^{j\phi} \cdot e^{j\omega t}\}$$

$$\operatorname{Re}\left\{\underbrace{(j\omega L + R)}_{\text{fazör}} \cdot I_m \cdot e^{j\beta} \cdot e^{j\omega t}\right\} = \operatorname{Re}\left\{\underbrace{V_m \cdot e^{j\phi}}_{\text{fazör}} \cdot e^{j\omega t}\right\}$$

$$(j\omega L + R) \cdot I_m \cdot e^{j\beta} = V_m \cdot e^{j\phi}$$

$$I_m \cdot e^{j\beta} = \frac{V_m \cdot e^{j\phi}}{(R + j\omega L)} \rightarrow I_m \frac{e^{j\beta}}{\text{kalıcı durum}}$$

$$\Rightarrow \operatorname{Re}\{I_m \cdot e^{j\beta} \cdot e^{j\omega t}\} \xrightarrow{P^{-1}} i_{ss}(t) = I_m \cdot \cos(\omega t + \beta)$$

$$V = V_1 + V_2 + V_3 + \dots + V_n$$

$$\bar{V} = \bar{V}_1 + \bar{V}_2 + \dots + \bar{V}_n$$

$$y_1 = 200 \cdot \cos(\omega t - 30^\circ) \quad y_2 = 40 \cdot \cos(\omega t + 60^\circ)$$

$$y_1 + y_2 = ? \rightarrow \bar{y}_1 + \bar{y}_2 = 20 \angle -30^\circ + 40 \angle 60^\circ$$



$$(17.32 - j10) + (20 + j34.64)$$


$$= 37.32 + j24.64 = 44.72 \angle 33.48^\circ$$



$$y_1 + y_2 = 44.72 \cdot \cos(\omega t + 33.48^\circ)$$

Fazör Bölgelerinde Pasif Devre Elemanları

Direnç

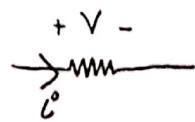


$$i = I_m \cdot \cos(\omega t + \phi_i)$$

$$V = R \cdot I_m \cdot \cos(\omega t + \phi_i)$$

$$\boxed{\bar{V} = R \cdot I_m \angle \phi_i} \rightarrow I_m \angle \phi_i : \text{ akımın fazör gösterimi}$$

$$\bar{V} = R \cdot \bar{I}$$

İndüktör

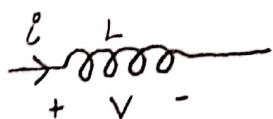

$$i = I_m \cdot \cos(\omega t + \phi_i) \rightarrow I_m \angle \phi_i$$

$$V = L \cdot \frac{di}{dt} = -\omega L I_m \cdot \sin(\omega t + \phi_i)$$

$$\hookrightarrow -\omega L I_m \cdot \cos(\omega t + \phi_i - 90^\circ)$$

$$\hookrightarrow -\omega L \cdot I_m e^{j(\phi_i - 90^\circ)} = -\omega L \cdot I_m \angle \phi_i - 90^\circ$$

$$\hookrightarrow -\omega L \cdot I_m \cdot e^{j\phi_i} \cdot e^{-j90^\circ} \quad \overbrace{e^{-j90^\circ}}^{\rightarrow -j}$$

$$\hookrightarrow \frac{j\omega L I_m \cdot e^{j\phi_i}}{\bar{I}}$$

$$\bar{V} = j \cdot \omega L \cdot \bar{I} = (\omega L \angle 90^\circ) (I_m \angle \phi_i)$$

$$= \omega L \cdot I_m \angle \phi_i + 90^\circ$$

faz farkı ∇

Kapasitör

$$\rightarrow \begin{array}{c} i \\ | \\ | \\ + V - \end{array} \quad V = V_m \cdot \cos(\omega t + \phi_v) \longrightarrow V_m \cdot \angle \phi_v$$

$$i = C \cdot \frac{dV}{dt} = -C \cdot \omega \cdot V_m \sin(\omega t + \phi_v)$$

$$= -C \cdot \omega \cdot V_m \cdot \cos(\omega t + \phi_v - 90^\circ)$$

$$= -C \cdot \omega \cdot V_m \cdot e^{j(\phi_v - 90^\circ)} = -C \cdot \omega \cdot V_m \cdot e^{j\phi_v} \cdot \underbrace{e^{-j90^\circ}}_{-j}$$

$$= j \cdot C \cdot \omega \cdot V_m \cdot e^{j\phi_v}$$

$$= j \cdot C \cdot V_m \cdot \angle \phi_v$$

$$\overline{I} = j \cdot \omega C \cdot \frac{V_m \angle \phi_v}{V} \longrightarrow \overline{V} = \frac{\overline{I}}{j \cdot \omega C} = \frac{1}{j \cdot \omega C} \cdot I_m \angle \phi_v$$

$$= \frac{e^{-j90^\circ}}{\omega C} \cdot I_m \angle \phi_v$$

←

$$\overline{V} = \frac{I_m}{\omega C} \cdot \angle \phi_v - 90^\circ$$

Empedans Ve Reaktans

$$\bar{V} = R \cdot \bar{I}$$

direng

$$\bar{V} = j \cdot w \cdot L \bar{I}$$

indüktör

$$\bar{V} = \frac{1}{jwC} \cdot \bar{I}$$

Kapasitör

$$\hookrightarrow \bar{V} = Z \bar{I} \quad \longrightarrow Z = \frac{\bar{V}}{\bar{I}}$$

empedans

$$Z_R = R$$


$$Z_I = j \cdot w \cdot L \quad Z \rightarrow \text{Ohm (Karmaşık sayı, fazör değil)}$$

$$Z_C = \frac{1}{jwC}$$

$$Im\{Z\} = \text{Reaktans}$$

	Empedans	Reaktans
Direng	R	X
indüktör	jwL	wL
Kapasitör	$j(-1/wC)$	$-1/wC$

$$\bar{j} = -\frac{1}{j}$$

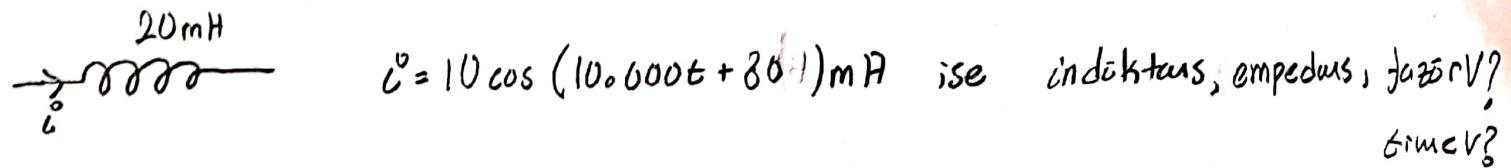


a) $\omega L = 200 \Omega$

b) $J\omega L = J200 \Omega$

c) $\bar{V} = J\omega L \cdot \bar{I} = J \cdot 10000 \cdot 20 \cdot 10^{-3} \cdot 10^{-2} / 30^\circ = J2 \angle 30^\circ = 2 \angle 120^\circ$

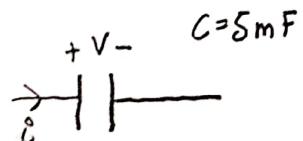d) $V(t) = 2 \cdot \cos(10000t + 120^\circ) \text{ V}$



$$V = 80 \cos(4000t + 25^\circ) \text{ V}$$

a) Reaktans $\rightarrow -1/(j\omega C) = -50 \Omega$


b) Empedans $\rightarrow -j/\omega C = -j50 \Omega$

c) Fazor Akim $\rightarrow \bar{I} = j\omega C \cdot \bar{V} = j \cdot 4000 \cdot 5 \cdot 10^{-3} \cdot 30 \angle 25^\circ = j60 \angle 25^\circ = 0,6 \angle 115^\circ$

d) $I(t) = 0,6 \cdot \cos(4000t + 115^\circ) \text{ A}$

Fazörlerde Devre Analizi

KVL-KCL

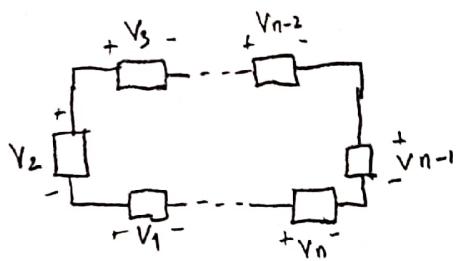

$$\bar{V}_1 + \bar{V}_2 + \bar{V}_3 + \dots + \bar{V}_n = 0$$




$$\bar{I}_1 + \bar{I}_2 + \bar{I}_3 + \dots + \bar{I}_n = 0$$

- Devreyi fazör bölgelere göre.
- Karmaşık ifadelerle analiz yap.
- Devreyi zaman bölgelere geri getir.

$$i_1 = 100 \cos(\omega t + 25^\circ) A$$

$$i_2 = 100 \cos(\omega t + 145^\circ) A$$
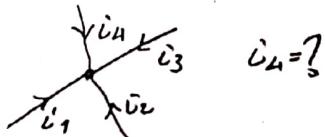
$$i_3 = 100 \cos(\omega t - 95^\circ) A$$



$$100 \angle 25^\circ = 100 e^{j25^\circ} = 100 (\cos 25^\circ + j \sin 25^\circ)$$


$$i_1 + i_3 + i_4 + i_2 = 0 \rightarrow \bar{I}_1 + \bar{I}_2 + \bar{I}_3 + \bar{I}_4 = 0$$

$$\hookrightarrow 100 \angle 25^\circ + 100 \angle 145^\circ + 100 \angle -95^\circ + \bar{I}_4 = 0$$

$$90.63 + j42.2 - 81.91 + j57.3 - 80.71 - j99.6 + \bar{I}_4 = 0$$


$$\bar{I}_4 = 0$$

Seri Empedans

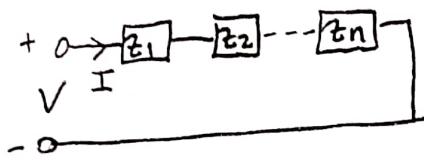

$$\bar{V} = Z_1 \cdot \bar{I} + Z_2 \cdot \bar{I} + Z_3 \cdot \bar{I} + \dots + Z_n \cdot \bar{I} = \bar{I} (Z_1 + Z_2 + Z_3 + \dots + Z_n) = \bar{I} Z_{eq}$$

$$Z_{eq} = \frac{\bar{V}}{\bar{I}}$$

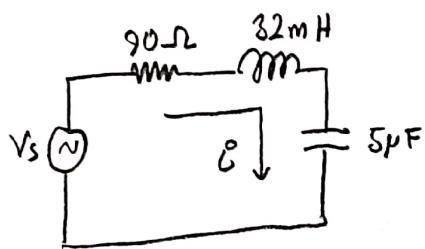


$$Z_R = R = 90 \Omega$$

$$Z_L = j\omega L = j \cdot 160 \Omega$$

$$Z_C = -j/\omega C = -j40 \Omega$$

$$\bar{V}_s = 750 \angle 30^\circ$$

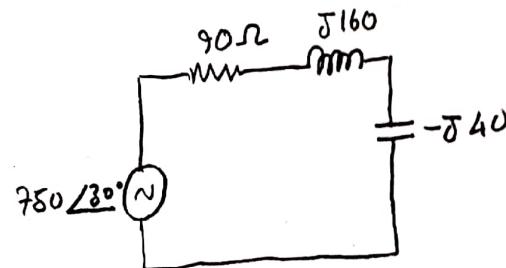

$$Z_{ab} = 90 + j160 - j40 = 90 + j120 \Omega$$


$$= 180 \angle 53.13^\circ$$

$$\bar{I} \cdot Z_{ab} = \bar{V}$$

$$\bar{I} = \frac{750 \angle 30^\circ}{180 \angle 53.13^\circ} = 5 \angle -23.13^\circ A$$


$$i(t) = 5 \cos(5000t - 23.13^\circ) A$$

Parallel Impedances

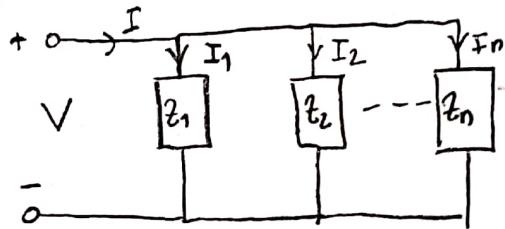

$$\bar{I} = \bar{I}_1 + \bar{I}_2 + \bar{I}_3 + \bar{I}_4 + \dots + \bar{I}_n$$
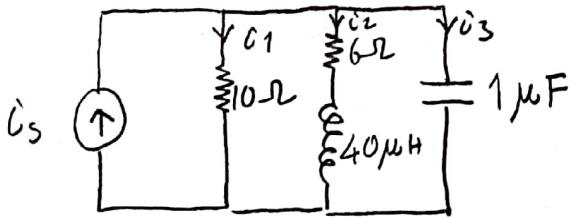
$$\frac{\bar{V}}{Z_{eq}} = \bar{V} \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots + \frac{1}{Z_n} \right) \quad \xrightarrow{Z_{eq}}$$



$$U_s = 8 \cos(200,000t) \text{ V}$$


$$U_s = 8 \angle 0^\circ$$

$$Z_{10} = 10 \Omega$$

$$Z_6 = 6 \Omega$$

$$Z_{A0} = j\omega L = j8 \Omega$$

$$Z_1 = -j5 \Omega$$

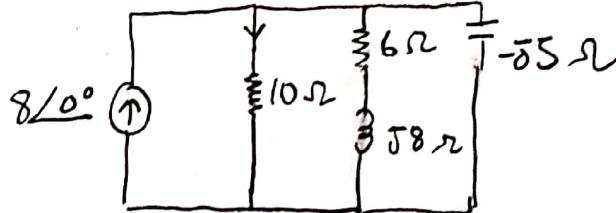

$$\frac{1}{Z_{eq}} = \frac{1}{10} + \frac{1}{j8+6} - \frac{1}{j5} = 4-j3 \Omega$$

$$|Z_{eq}| = \sqrt{4^2 + (-3)^2} = 5$$

$$\angle Z_{eq} = \tan^{-1}\left(\frac{-3}{4}\right) = -36.87^\circ$$




$$Z_{eq} = 5 \angle -36.87^\circ$$

$$\bar{V} = Z_{eq} \cdot \bar{I} = 5 \angle -36.87^\circ \times 8 \angle 0^\circ = 40 \angle -36.87^\circ$$

$$V(t) = 40 \cos(200,000t - 36.87^\circ) \text{ V}$$

Anlık ve Ortalama Güç

$$P=V \cdot I$$

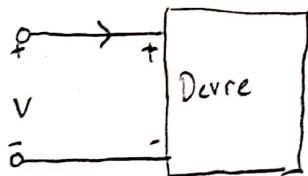

$$\bullet P(t) = V(t) \cdot I(t)$$

$$V(t) = V_m \cos(\omega t + \theta_v)$$

$$I(t) = I_m \cos(\omega t + \theta_i)$$

$$P(t) = V_m \cdot I_m \cdot \cos(\omega t + \theta_v) \cdot \cos(\omega t + \theta_i)$$

$$= \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)]$$

$$P(t) = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)$$

\downarrow
Anlık güç

$$\hat{P} = \frac{1}{T} \cdot \int_0^T P(t) dt = \frac{V_m \cdot I_m}{2} \cos(\theta_v - \theta_i) = \frac{1}{2} \operatorname{Re} [\bar{V} \cdot \bar{I}^*]$$

$$V(t) = 120 \cos(377t + 45^\circ) V, \quad I(t) = 10 \cos(377t - 10^\circ) A$$

$$\text{anlık güç} = V(t) \cdot I(t) = 600 (\cos(55) + \cos(754t + 35)) W$$

\downarrow
ortalama güç